# Lecture 24 EE 421 / C\$ 425 Digital System Design

Fall 2023
Shahid Masud




# Topics

- Recap: BIST and its Components
- SISR Serial Input Shift Signature Register
- MISR Multi Input Signature Register
- BILBO Built-In Logic Block Observer
- Boundary Scan
- JTAG Standard

QUIZ 5 today




# Recap: Designing with BIST Circuits

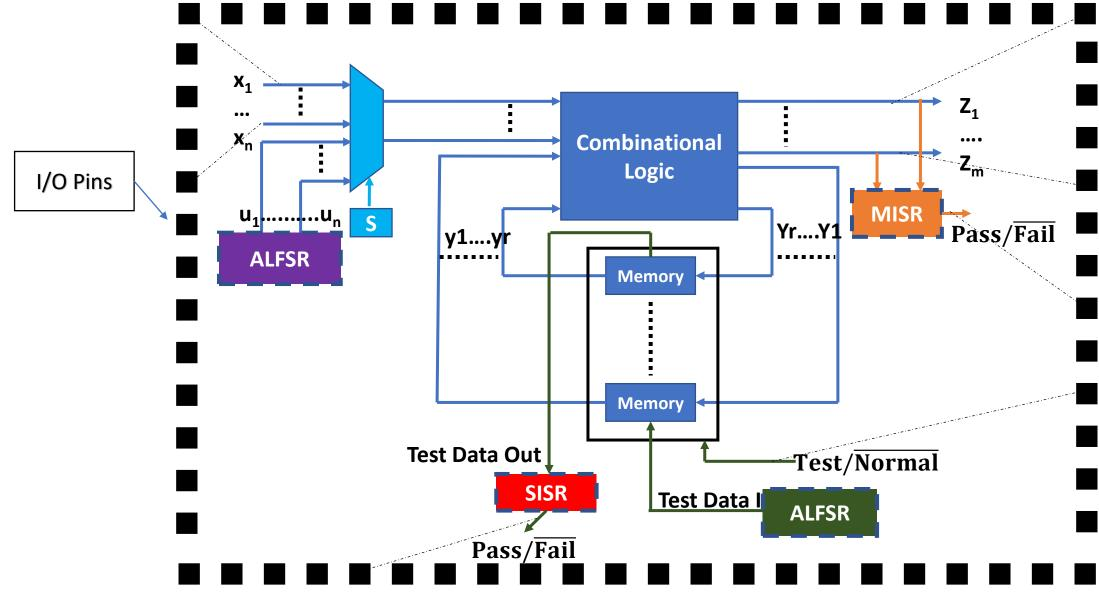



# SISR – Serial Input Shift Register

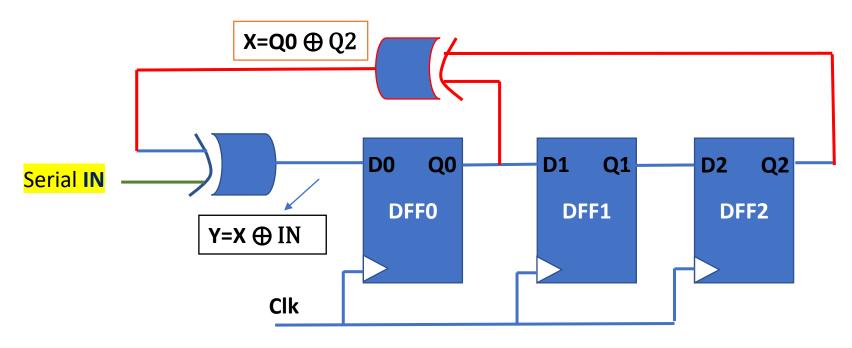

- The flip flops and feedback XOR gate form an ALFSR with some seed value
- The output from XOR is taken through another XOR with Serial IN bit stream
- The circuit continues to advance one bit at a time, with each clock edge
- Once all bits have been read through Serial IN, final status of Q0, Q1, and Q2 represents a signature pattern
- The pattern will only re-appear if the same bit pattern is presented at input
- No other pattern will produce the same final signature output at registers



# SISR Example


Eg., Let seed value = '000'
Generate Signature for input bit patterns '011101"

	<b>P</b>				<b>,.</b>	_
Clk	IN	X	Υ	Q0	Q1	Q2
1	0	0	0 \	0	0 \	0
2	1	0	1	0	0	0
3	1	1	0	1	0	0
4	1	0	1 \	0	1	0
5	0	0	0	1	0	1
6	1	0	1	0	1	0
7	END			1	0	1

Signature produced



# SISR – Serial Input Signature Register

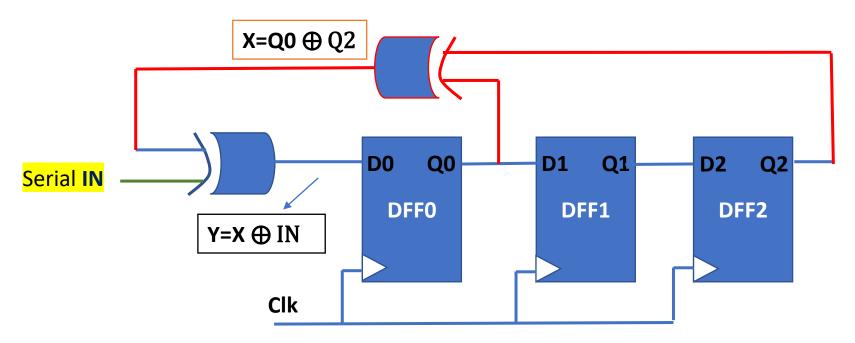


- The flip flops and feedback XOR gate form an ALFSR with some seed value
- The output from XOR is taken through another XOR with Serial IN bit stream
- The circuit continues to advance one bit at a time, with each clock edge
- Once all bits have been read through Serial IN, final status of Q0, Q1, and Q2 represents a signature pattern
- The pattern will only re-appear if the same bit pattern is presented at input
- No other pattern will produce the same final signature output at registers


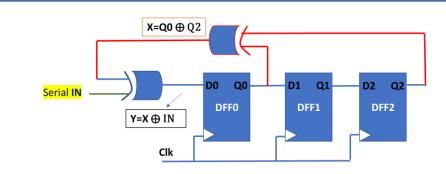
# SISR Example

Eg., Let seed value = '000' Generate Signature for input bit patterns '011101"





	<b>(P)</b>				<b>,.</b>	
Clk	IN	X	Y	Q0	Q1	Q2
1	0	0	0	0	0	0
2	1	0	1	0	0	0
3	1	1	0	1	0	0
4	1	0	1	0	1	0
5	0	0	0	1	0	1
6	1	0	1	0	1	0
7	END			1	0	1

Signature produced



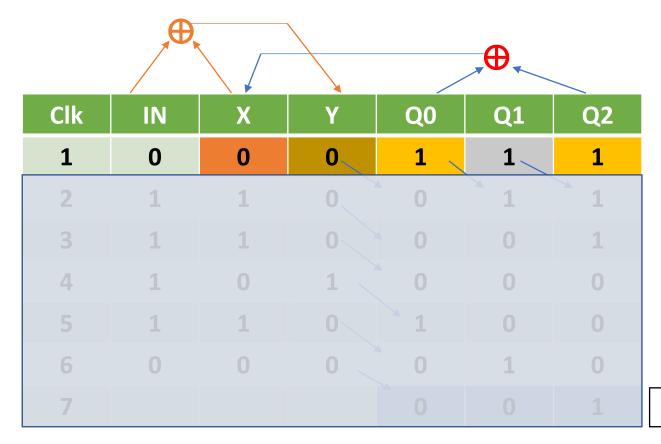
SISR Example 2 – Use sequence '011110', Seed value '111'



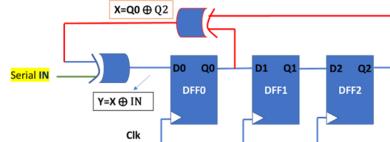

Final Signature

# MISR – Multi Input Signature Register

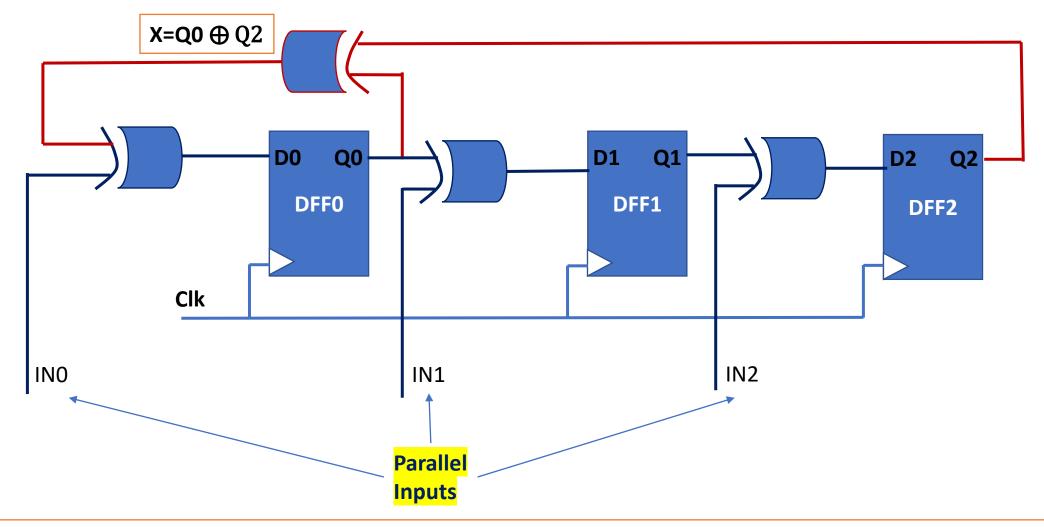

After all parallel inputs have been applied, one input set on each clock, the last status at Q0,Q1,Q2 is the signature

Example: Determine 'signature' when inputs {010, 101, 110, 111, 011} are applied at {IN0,IN1,IN2}




# BILBO – Built-In Logic Block Observer

- Combine the following into one circuit:
  - Pseudo Random Pattern Generator (ALFSR)
  - Serial Input Signature Register (SISR)
  - Multi-Input Signature Register (MISR)
  - Scan Registers



# **BILBO Implementation with 3 Registers**

$B_1$	$B_2$	Operation mode
1	1	Normal
0	0	Scan
1	0	Mixed Test Generation and Signature Analysis
0	1	Reset

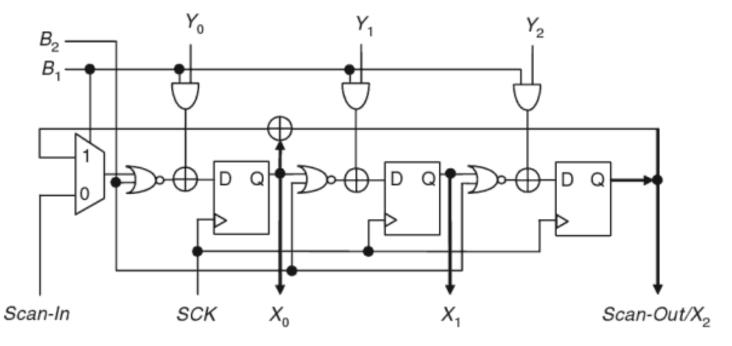





# Circuit Example

B1	B2	Operating Mode
0	0	Shift Register
0	1	PR PG (Pattern Gen)
1	0	Normal
1	1	MISR

### **Line Colour**

Red = feedback ALFSR

**Orange** = Control Selection


Navy Blue = MISR

Green = Scan Chain Sin to Sout

Brown = Select MUX input


Red and Green = SISR

PR PG = Pseudo Random Patr Gen

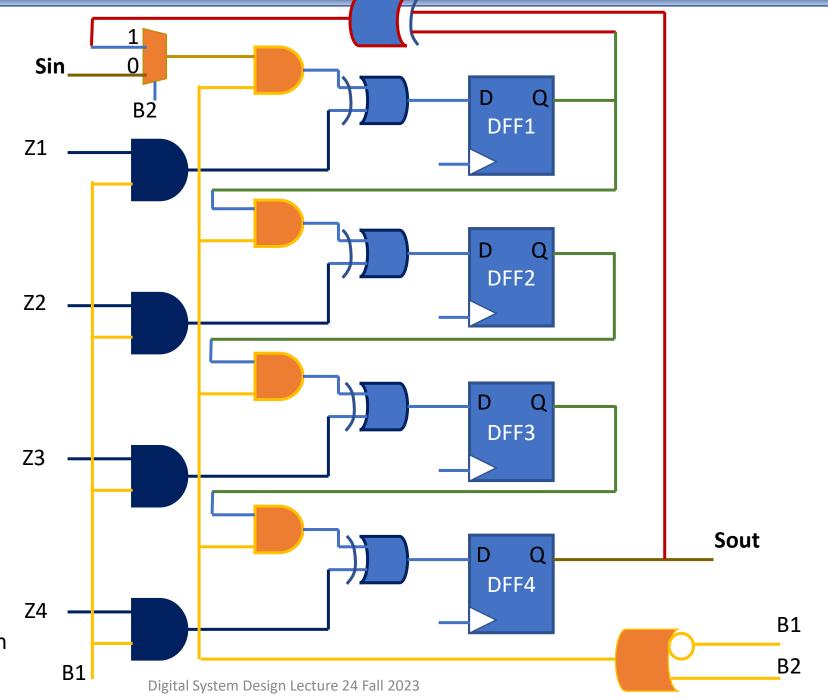



# **BILBO** Application

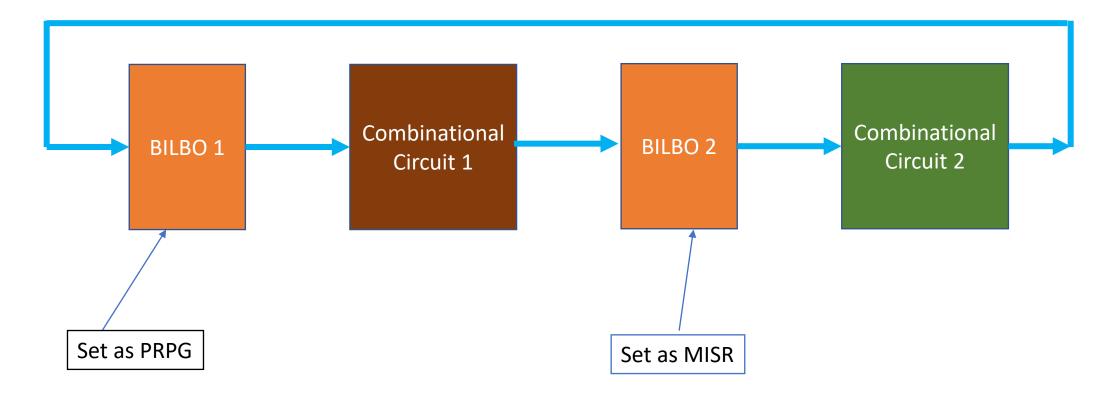


To Test Combinational Circuit 1, BILBO 1 is used as PRPG and BILBO 2 is used as MISR In the Normal mode, both BILBO serve as registers for associated combinational logic block To Scan data IN and OUT, both BILBO operate in Shift Register mode



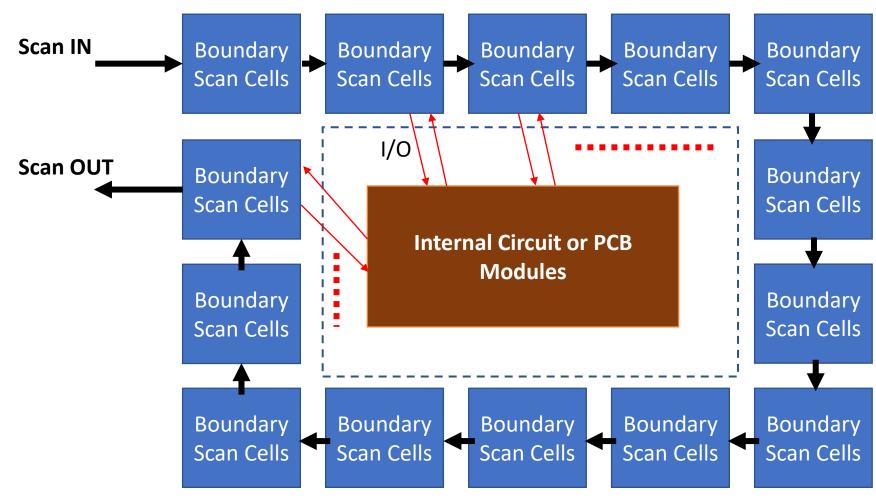
# **Boundary Scan – Concept**

Place Scan cells along the boundary I/O Ports of an ASIC or PCB. They can be connected in the <u>form of a Scan</u> <u>Chain</u> to <u>apply test vectors to internal circuit</u> or <u>PCB modules</u>.





# Boundary Scan Implementation

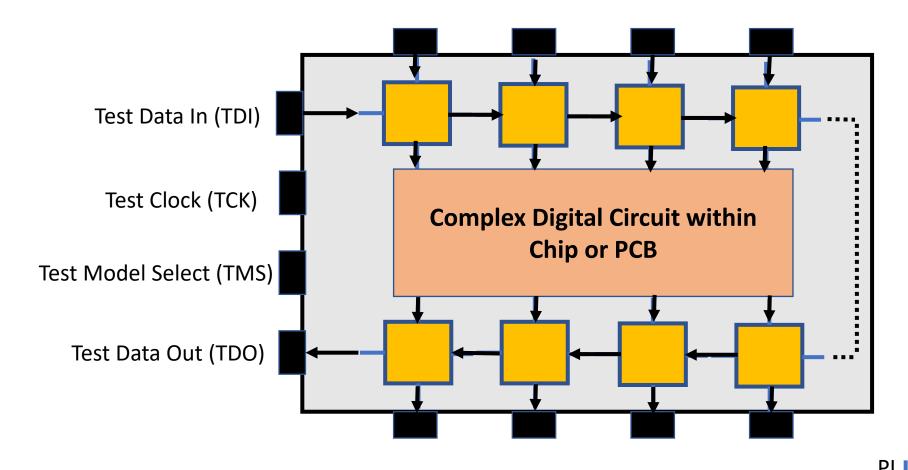

PI = Parallel In

PO = Parallel Out

SI = Serial IN


SO = Serial OUT Digital System Design Lecture 24 Fall 2023

A Boundary Scan Cell

PO\*



SO

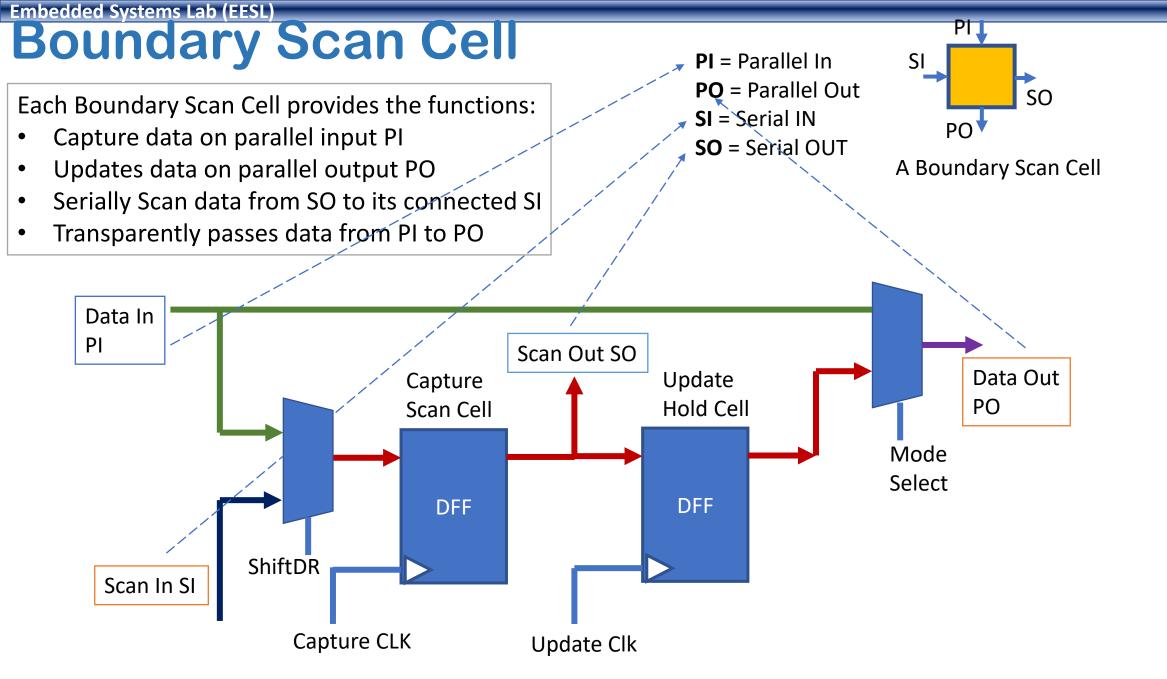



# **Boundary Scan Cell – Modes of Operation**

Normal / Transparent: Data In (PI) is passed Out to Data Out (PO)

Capture: Test Data In will be captured into the

'Capture Scan Cell' in next Capture Clk

**Update:** Data stored in 'Capture Scan Cell' is


propagated to 'Update Hold Cell' when

Update Clk appears

Serial Shift: Test data is shifted from Serial In (SI)


and test response can be scanned through

Serial Out (SO)

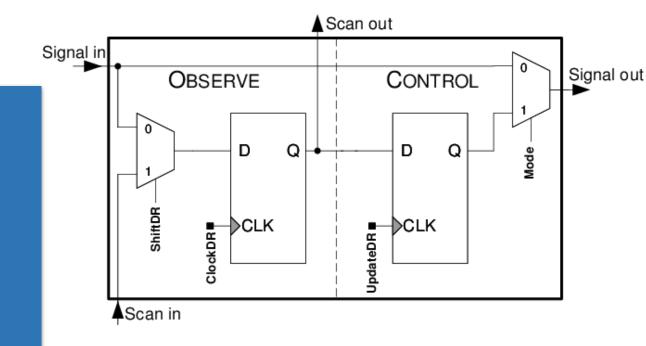


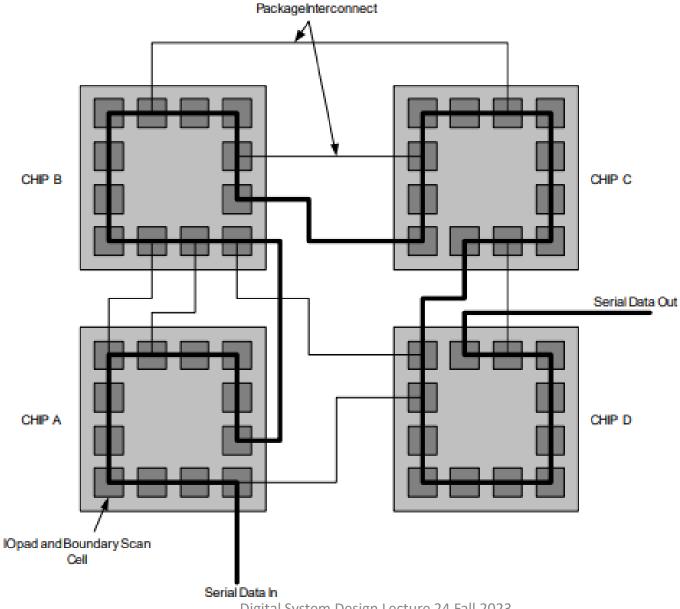
# Boundary Scan Example - Testing Multiple Chips





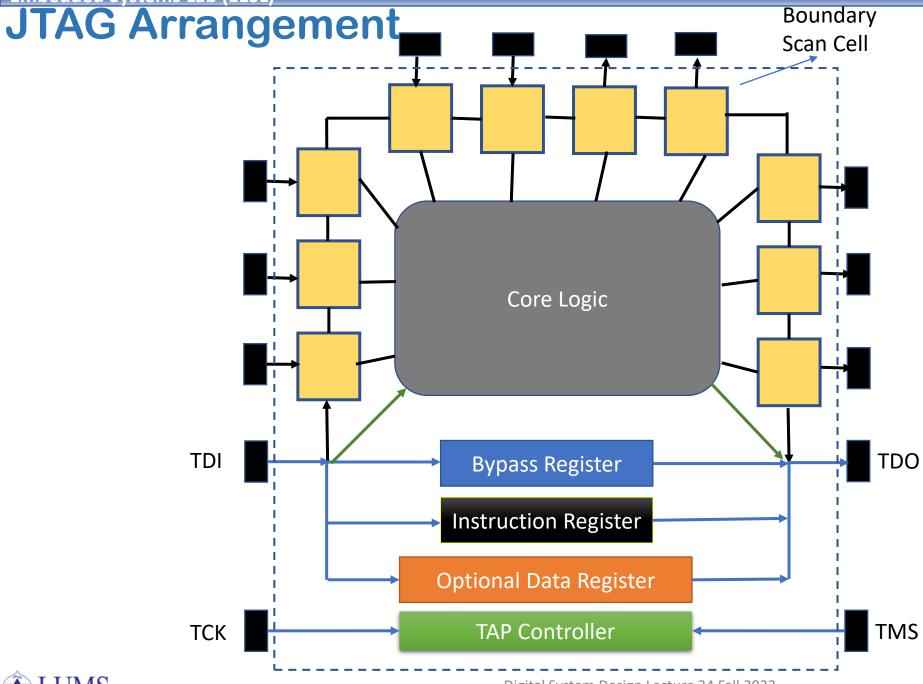
# **JTAG Standard**


- IEEE Joint Test Action Group (JTAG) Standard 1149.1 was finalized in 1990. Latest release was in 2001
- The standard is based on Boundary Scan and Test Access Port architecture
- Allows complete controllability and observability of the boundary pins of a JTAG compatible device under software control
- During test modes, all input signals are captured for analysis and all output signals are preset to test internal devices.
- The operation of these scan cells is software controlled through the Test Access Port (TAP) Controller and the instruction register
- See block diagram next page







# **JTAG**

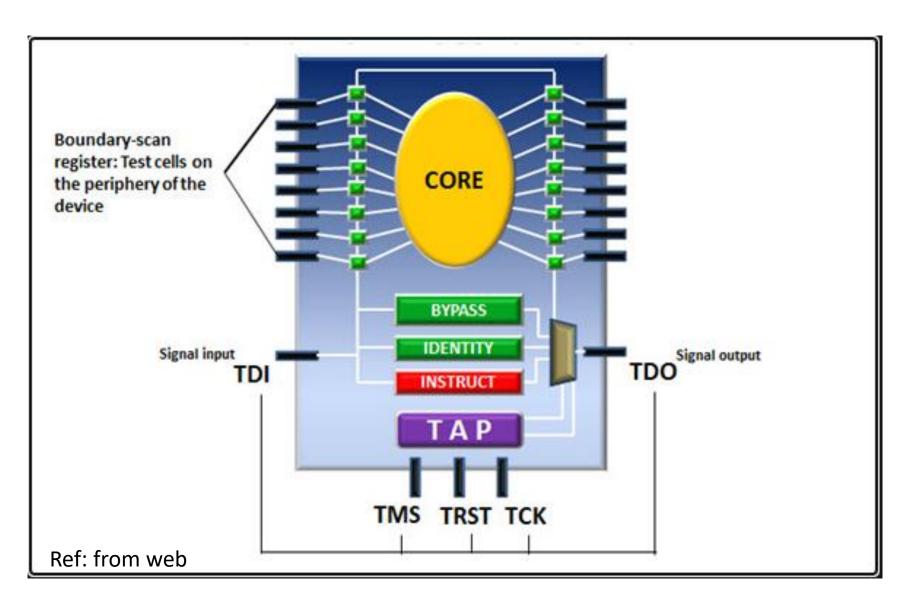

Ref: from web



# Test Signals in JTAG TAP – Test Access Port

4 or 5 Pin connections are provided for TAP – Test Access Port

**TDI:** Test Data Input, this data is sifted serially into Boundary Scan Registers

**TCK:** Test clock signal


TMS: Test Mode Select

**TDO:** Test Data Out, this is serial output from Boundary Scan Registers

**TRST:** Test Reset, resets the TAP controller and test logic, optional pin



Im ) d J d S ys t m s & t (E. J.)

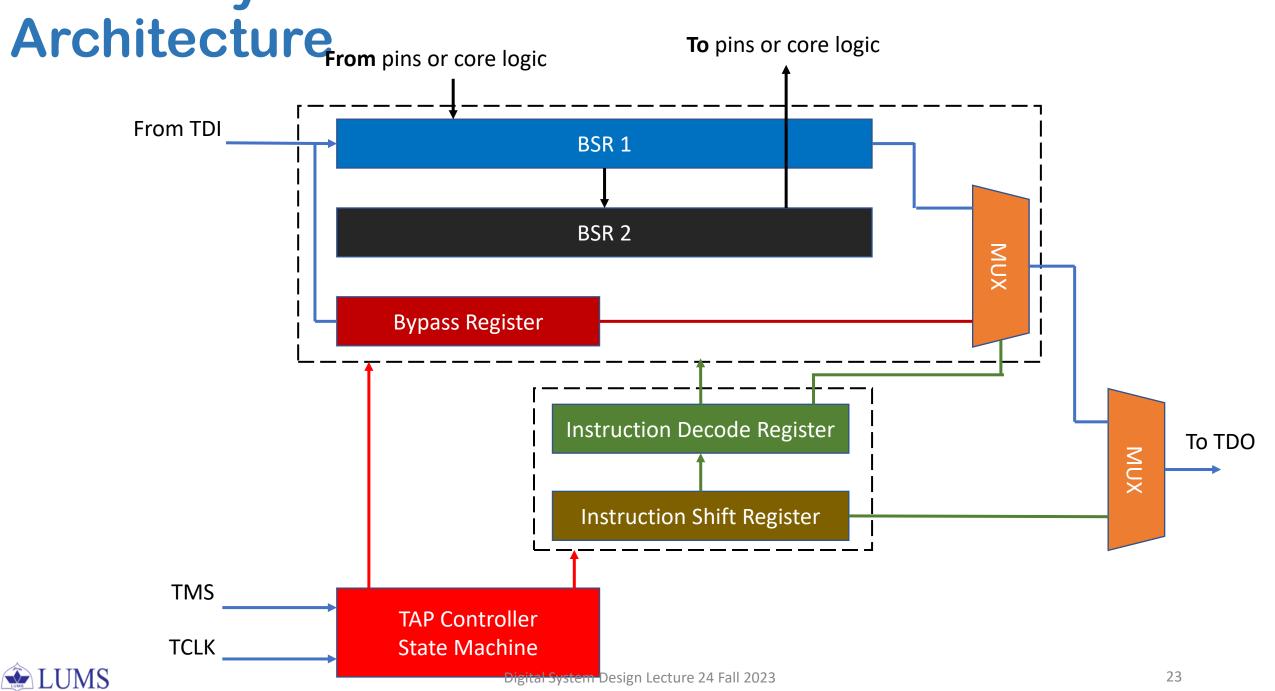

## asic JTAG Instructions

BYPASS: This instruction allows TDI serial data to through a 1-bit Bypass register on the IC instead of boundary can registers. In this way, one or more IC on the PCB may be bypassed while other IC are being tested.

SAMPLE/PRELOAD: This instruction is used to scan (read) the boundary scan registers without interfering with the normal operation of core logic. Data is transferred to or from the core logic from or to the IC pins without interference. Test data can be shifted into the BSR.

EXTEST: This instruction allows board-level interconnect testing. Test data is shifted into the BSR and then it goes to the output pins. Data from the input pins is captured by the BSR.


INTEST (optional): To test core logic, data shifted into BSR takes place of data from input pins, and output data from core logic is loaded into BSR.

RUNBIST (optional): This instruction causes special BIST logic within the IC to execute. PRPG, SISR and MISR can be invoked.


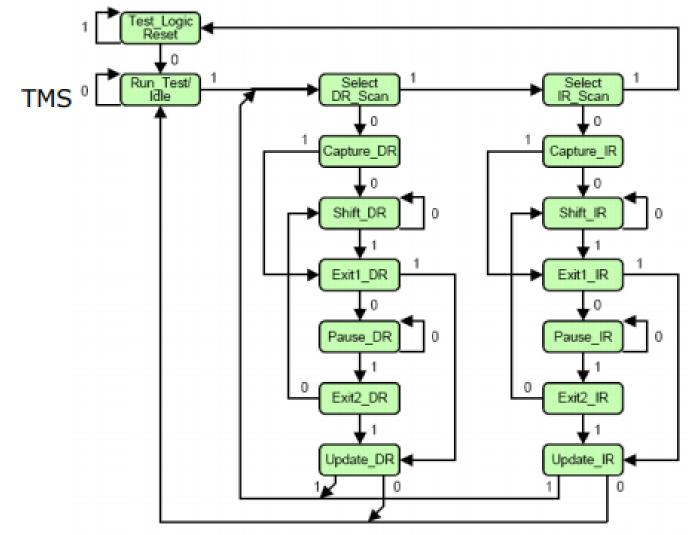
### Standard


A state transition occurs on the positive edge of TCK, and the controller output changes on the failing edge of the TCK





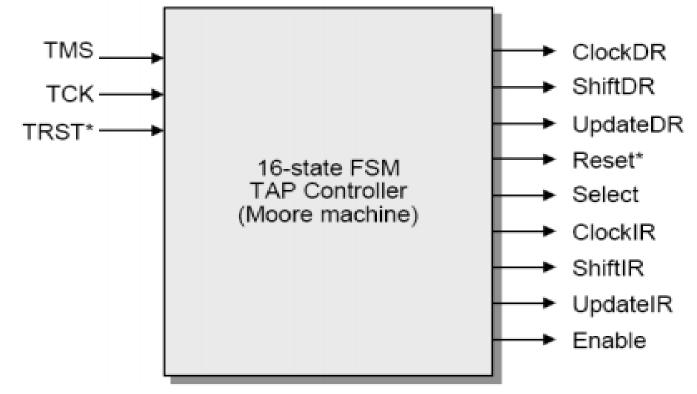
### **TAP Controller**

- 16 finite state machine which produce the various control signals
  - Dedicated signals to IR (ClockIR, ShiftIR, UpdateIR)
  - Dedicated signals to DR (ClockDR, ShiftRD, UpdateDR)
  - Reset\*: distributed to IR and targeted DR
  - Select: distributed to output mux
  - Enable: distributed to output drive amplifier





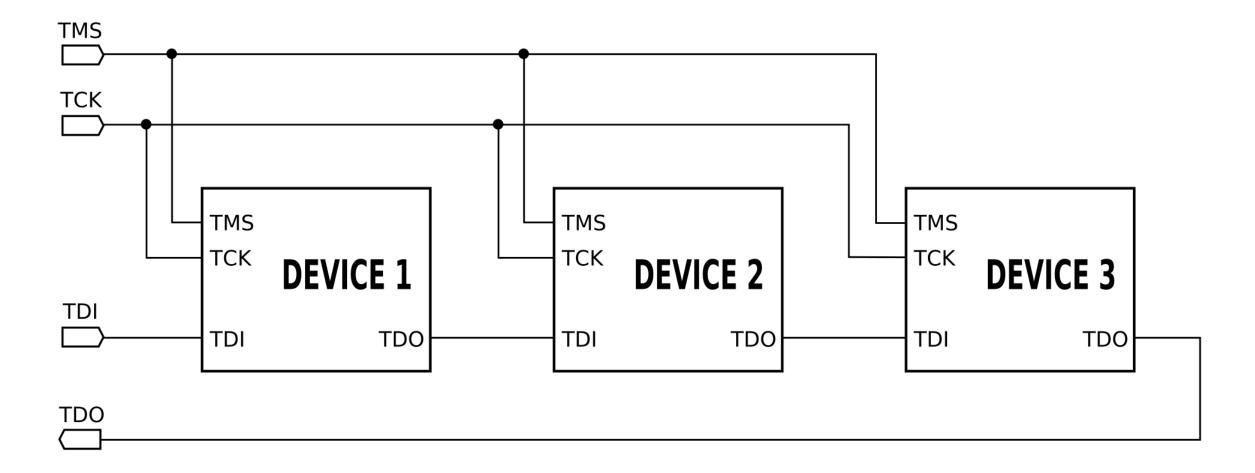
# Daisy Chain JTAG – for multiple devices






# **Testing Chip Interconnections**

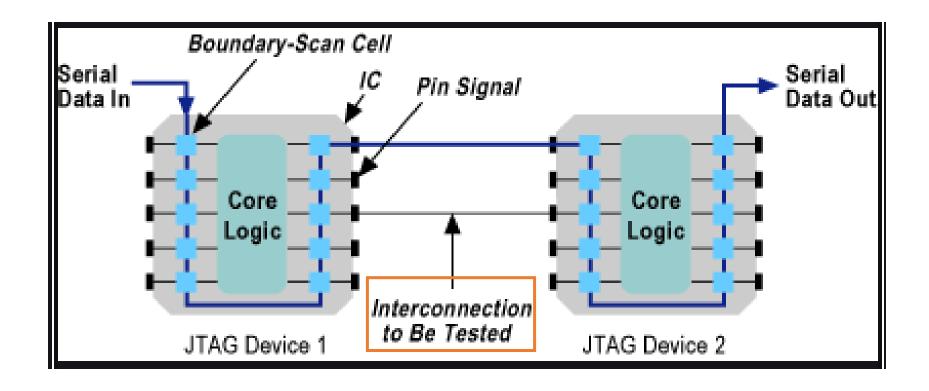

Pre-load the data on BSR of IC1
Transfer through PCB connections to IC2
Read the data from BSR of IC2



# TAP Controller for multiple devices

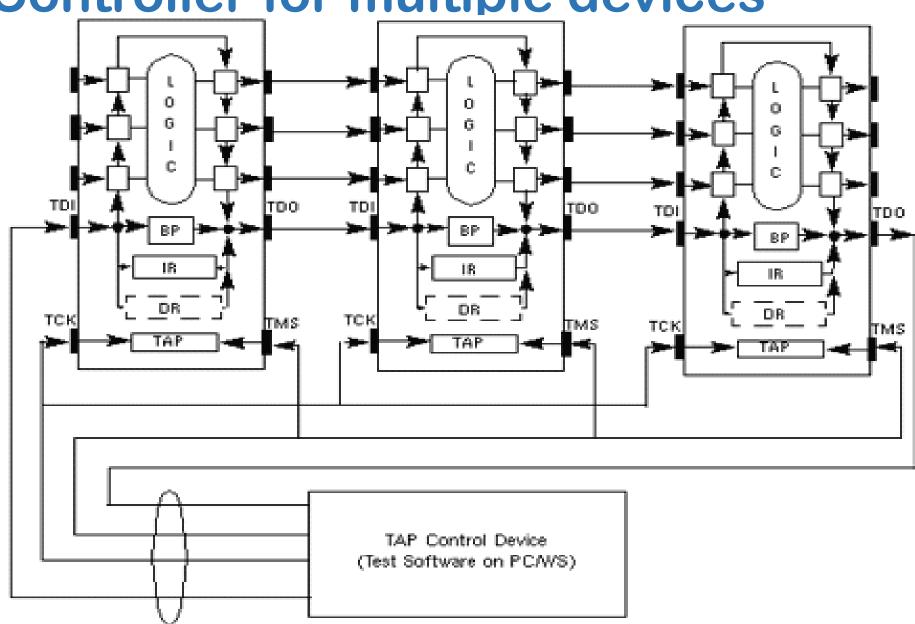

Ref: from web



Test Connector