

# Lecture 10

## EE 421 / CS 425

# Digital System Design



Fall 2023

Shahid Masud

# Topics

- Metastability
- Synchronizers for capturing Asynchronous Inputs
- Signal Transfer with and without Clock
- Communication between modules in Complex Digital System
- Quiz 2 today

  
# Objective – to reduce possible **Metastability** in capturing **Asynchronous Input**




**Synchronizer Failure: When flipflop hangs in a Metastable State for a long time (indefinitely)**

**Normally, the flipflop output would settle to a stable 0 or 1 state after some time**

# Output Behaviour with Metastability

 

 **DFF is connected to produce metastability  
As setup time is violated**



Oscilloscope trace of metastable behaviour


**Eventually a stable state is reached**

**Problem occurs when flipflop is not stable within  
One clock period**

# Synchronizers

- Asynchronous inputs are problematic as their transitions are not predictable
- High speed digital circuits rely on synchronizers to create a time buffer for recovering from a metastable event; thus reducing the possibility that metastability will cause circuit to malfunction
- An asynchronous signal should be synchronized by one synchronizer only. If not, then multiple synchronized signals could be present in the system and one of these could be driven into metastable state

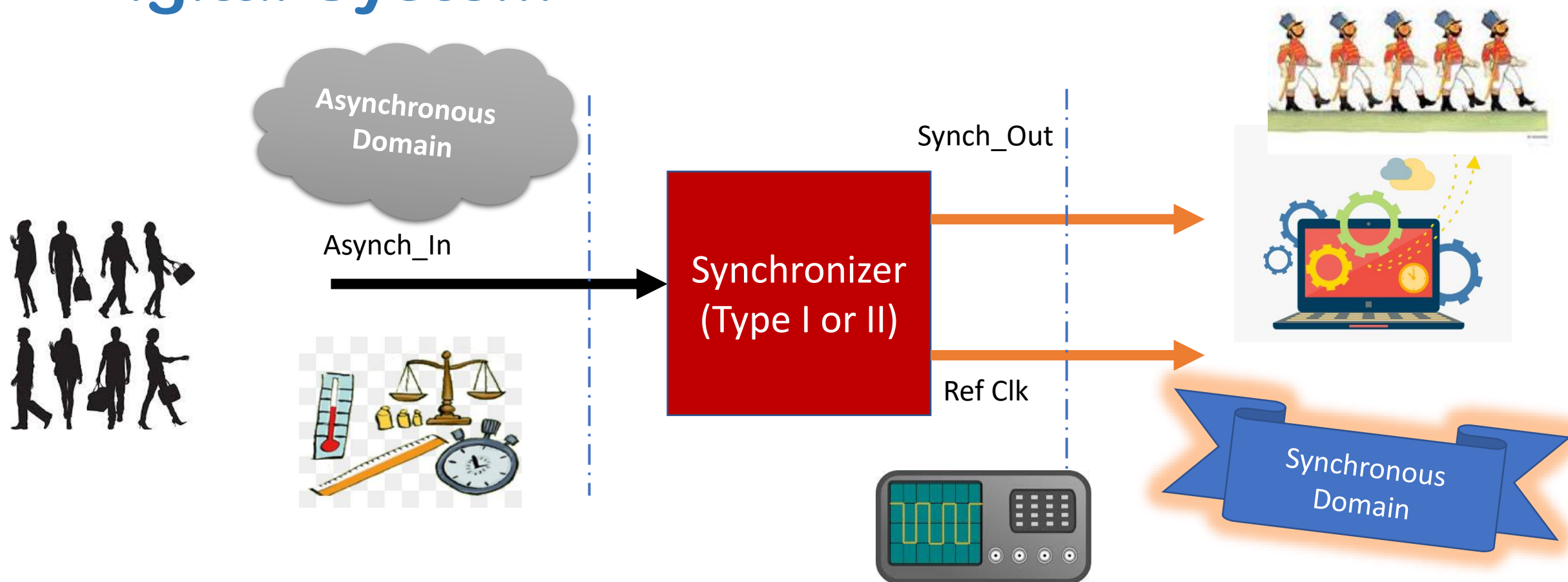
# Asynchronous Inputs to a Synchronous Digital System


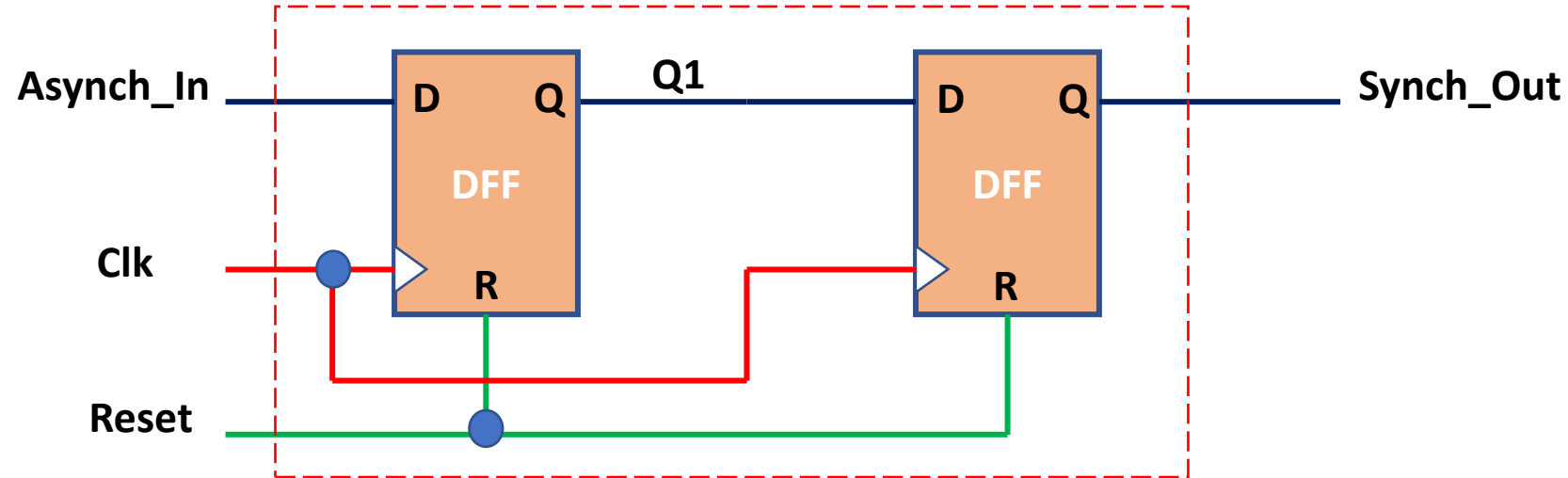
# Synchronizer 1


Condition: The width of asynchronous input pulse is greater than period of the clock

Synchronizer is a multistage shift register



Reset Input 'R' is used as control to bring Synch\_Out back to '0', as required


# Timing Diagram – Synchronizer 1

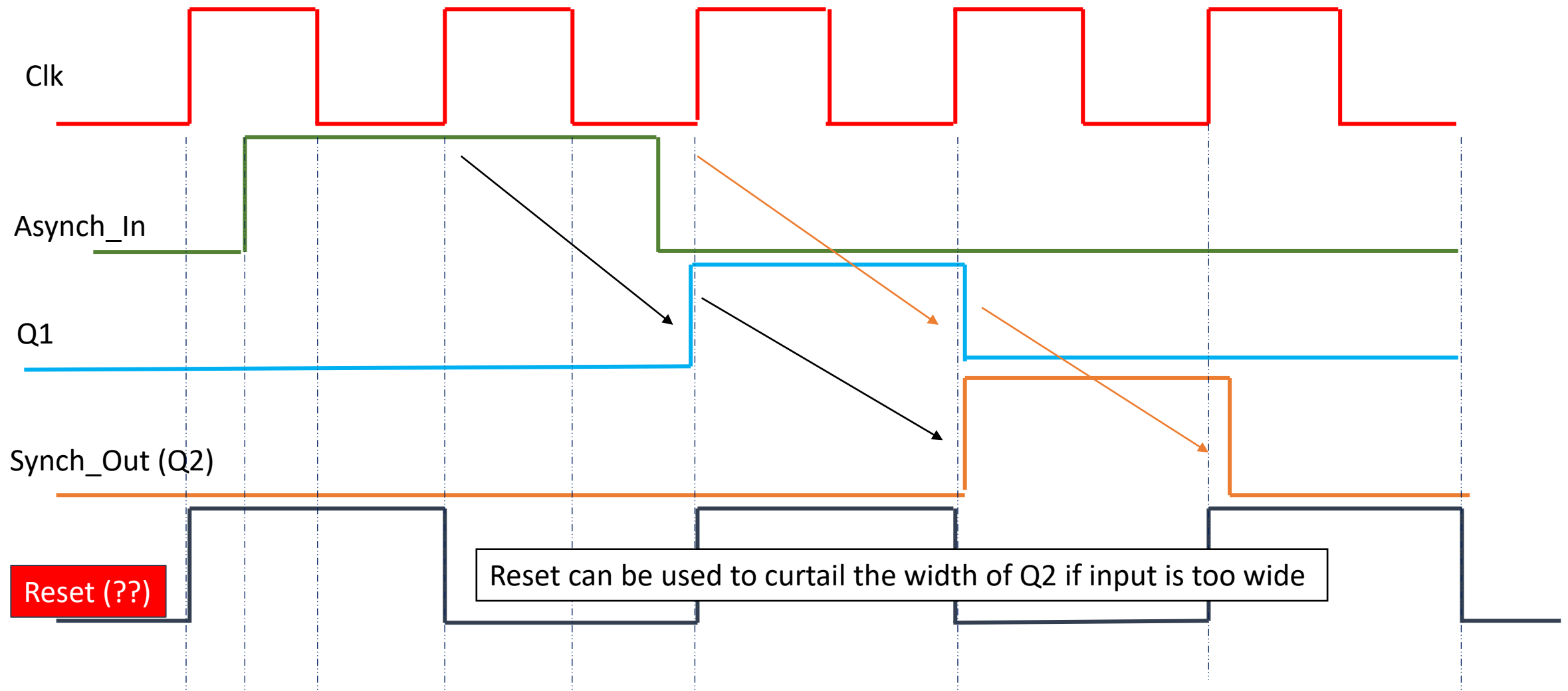




# Synchronizer 2

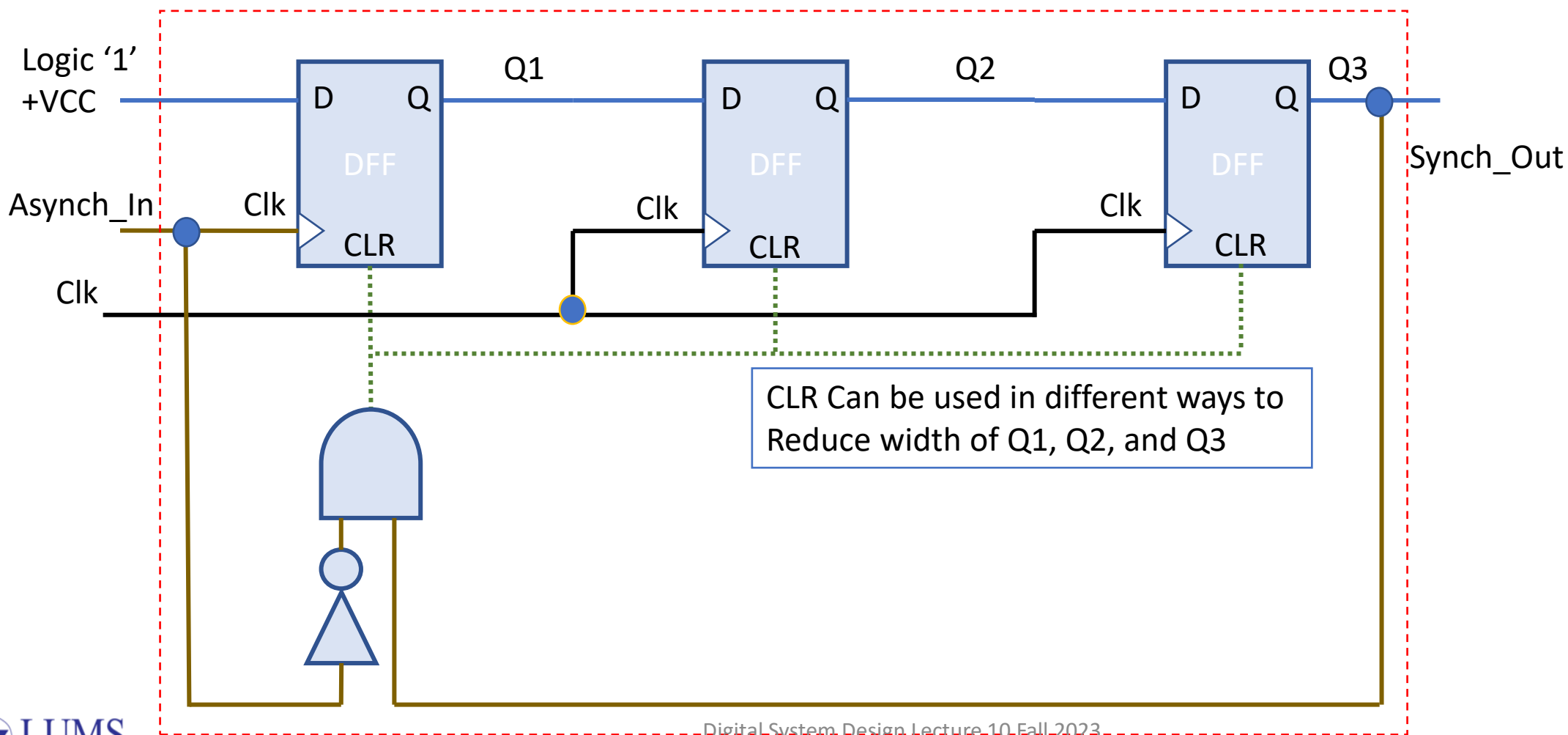**Condition: Width of the asynchronous input pulse is less than the period of the clock**



# Timing Diagram – Synchronizer 2

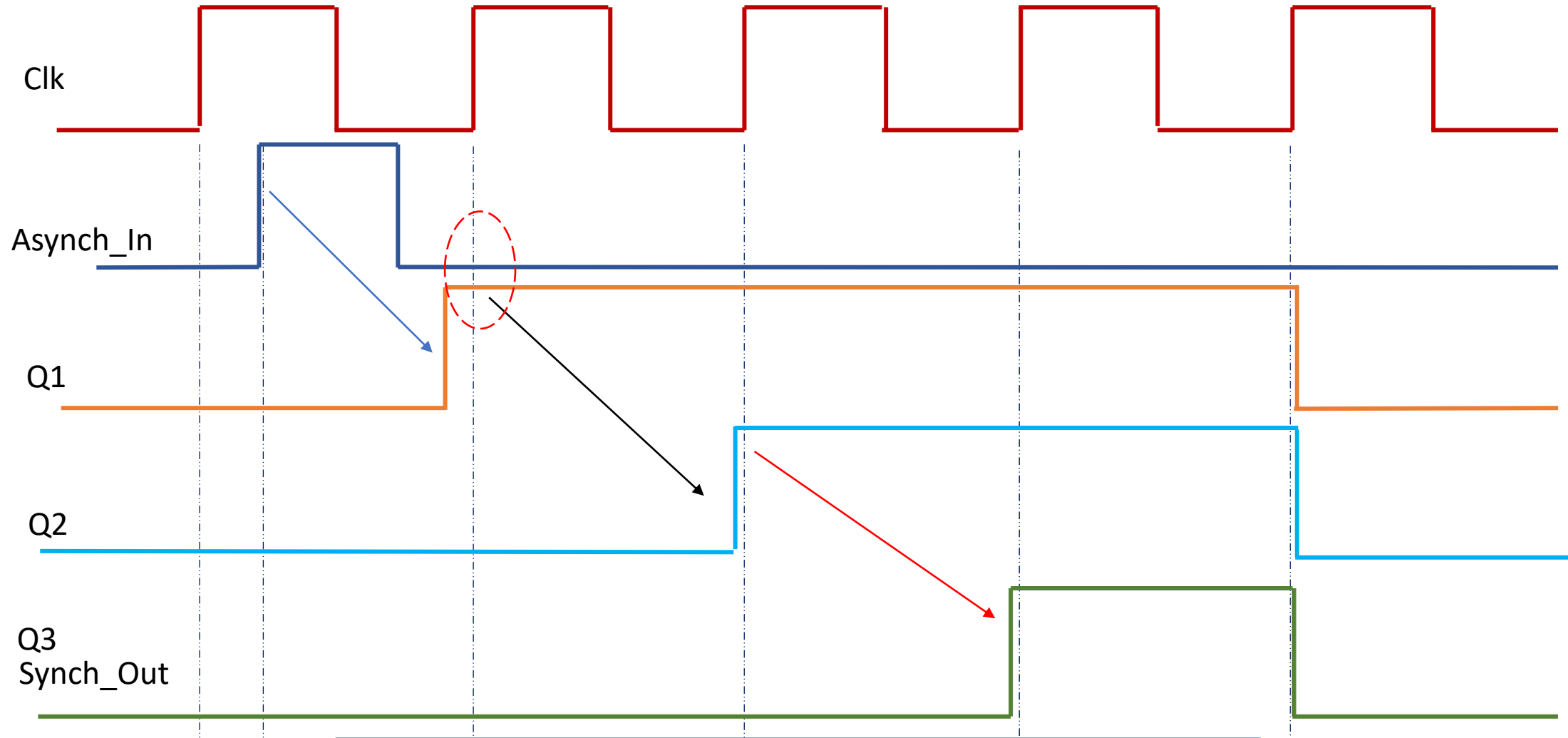


**CLR input at DFF1 is used to bring back Q1 and then Q2 to Zero**

# Self-Timed and Speed Independent Circuits

- Having a completed Synchronous system is at times too challenging for a complex and fast digital system
- The limiting problem becomes how to distribute a single global clock without introducing intolerable clock skew
- The alternate is to partition the digital system into locally clocked pieces that communicate with each other using delay-insensitive signaling techniques (i.e. local clock for local communication)
- Each block proceeds at its own speed without the need for a global clock, synchronizing local communication whenever needed
- Usually a Request-Response Signalling method is employed

# Data Reading across two Clock Domains

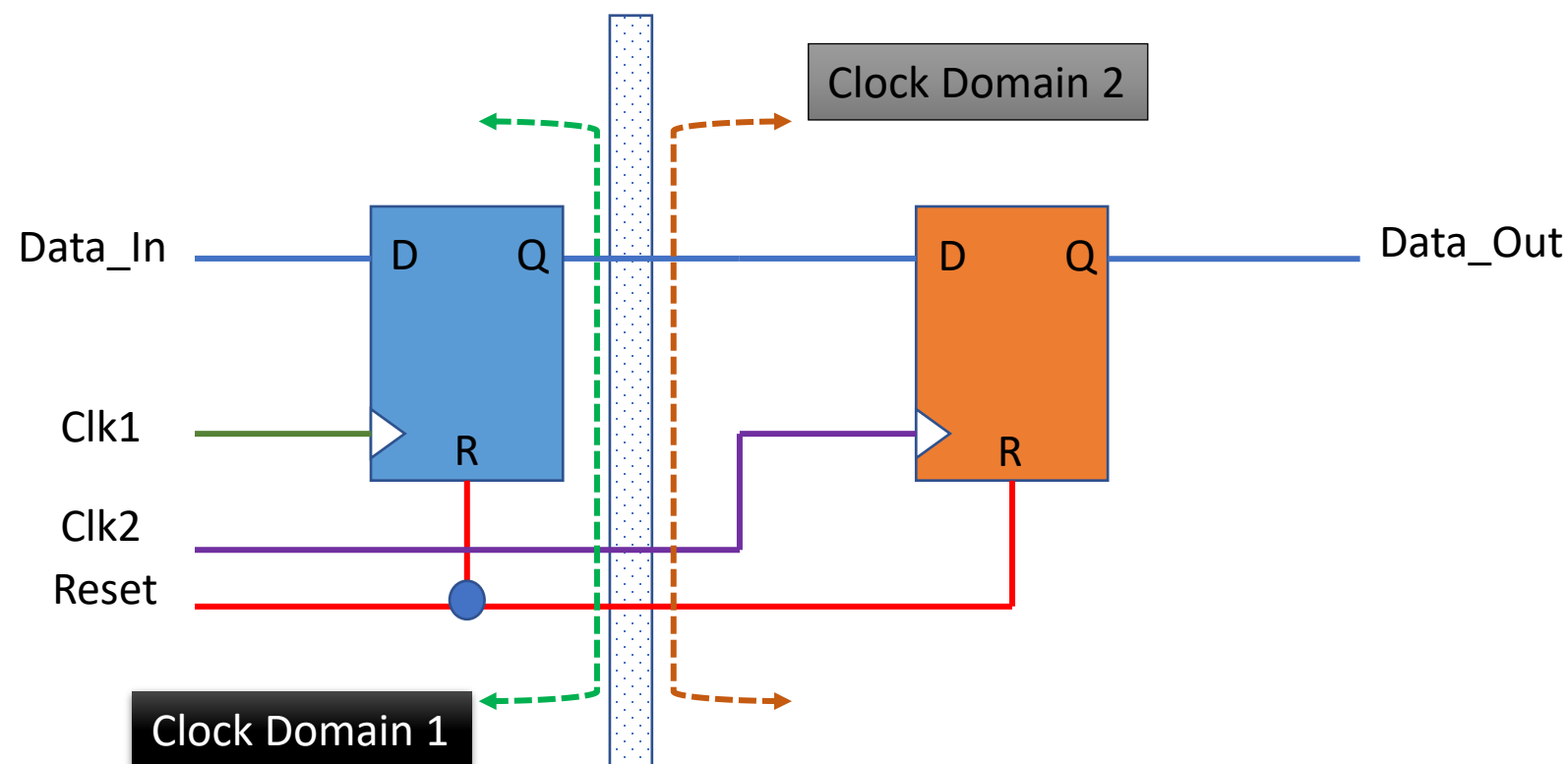

frequency of Clk1 is less than Clk2  
 Otherwise, the **Synchronizer-2** is versatile and can be used here

# Communication across modules in Complex SoC



- Communication Signaling across modules at different clock speeds
- Self-timed circuits

# Self-Timed and Speed Independent Circuits


- Having a completed Synchronous system is at times too challenging for a complex and fast digital system
- The limiting problem becomes how to distribute a single global clock without introducing intolerable clock skew
- The alternate is to partition the digital system into locally clocked pieces that communicate with each other using delay-insensitive signaling techniques (i.e. local clock for local communication)
- Each block proceeds at its own speed without the need for a global clock, synchronizing local communication whenever needed
- Usually a Request-Response Signaling method is employed

# Request / Acknowledge Signaling

Independently clocked Subsystems

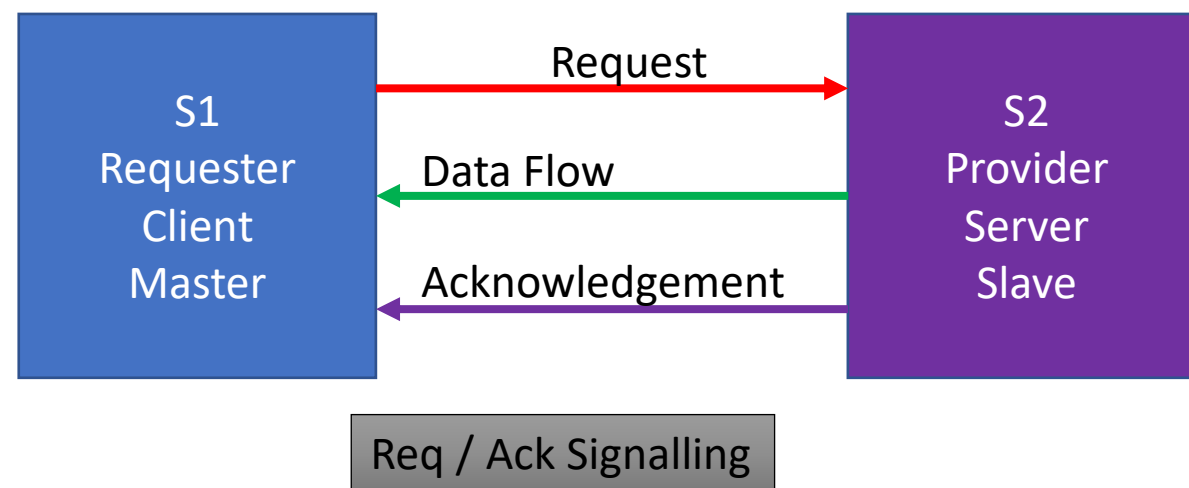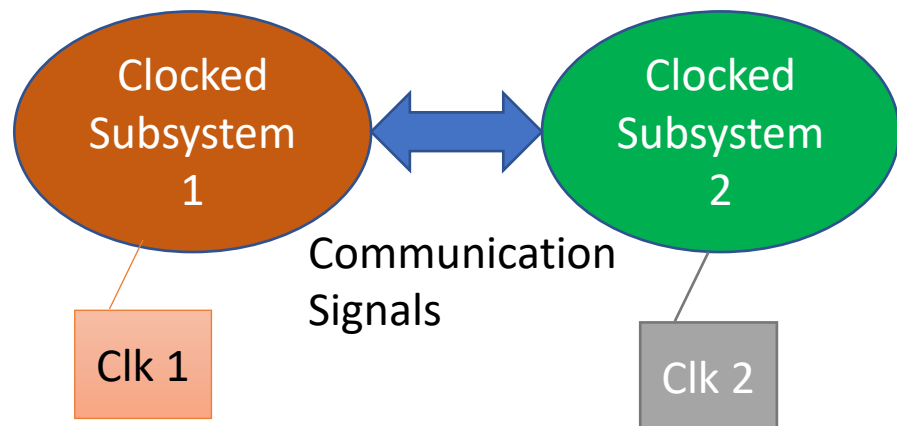


# Synchronous Req / Ack Signaling

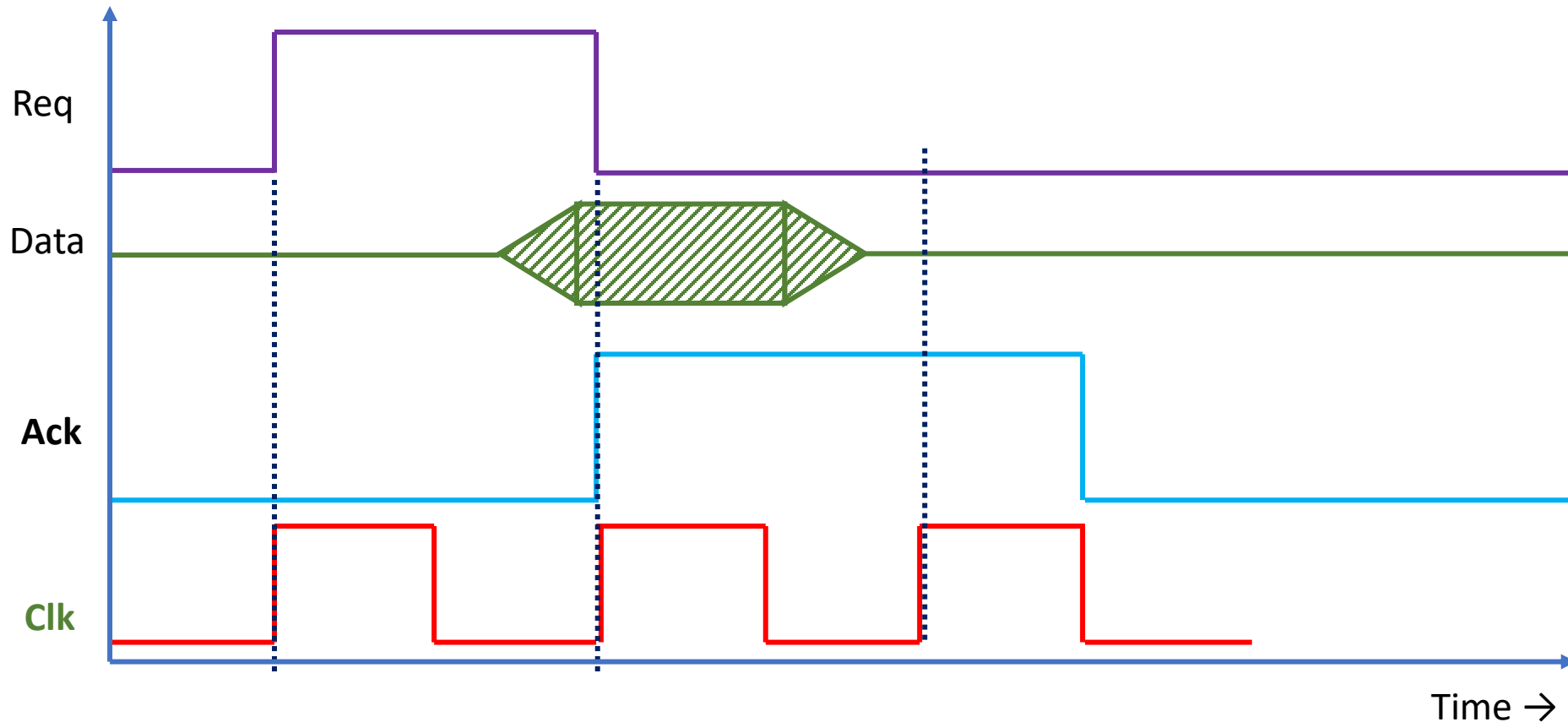

Req and Ack signals are synchronized to **Clk**




# Synchronous Req with Wait Signaling

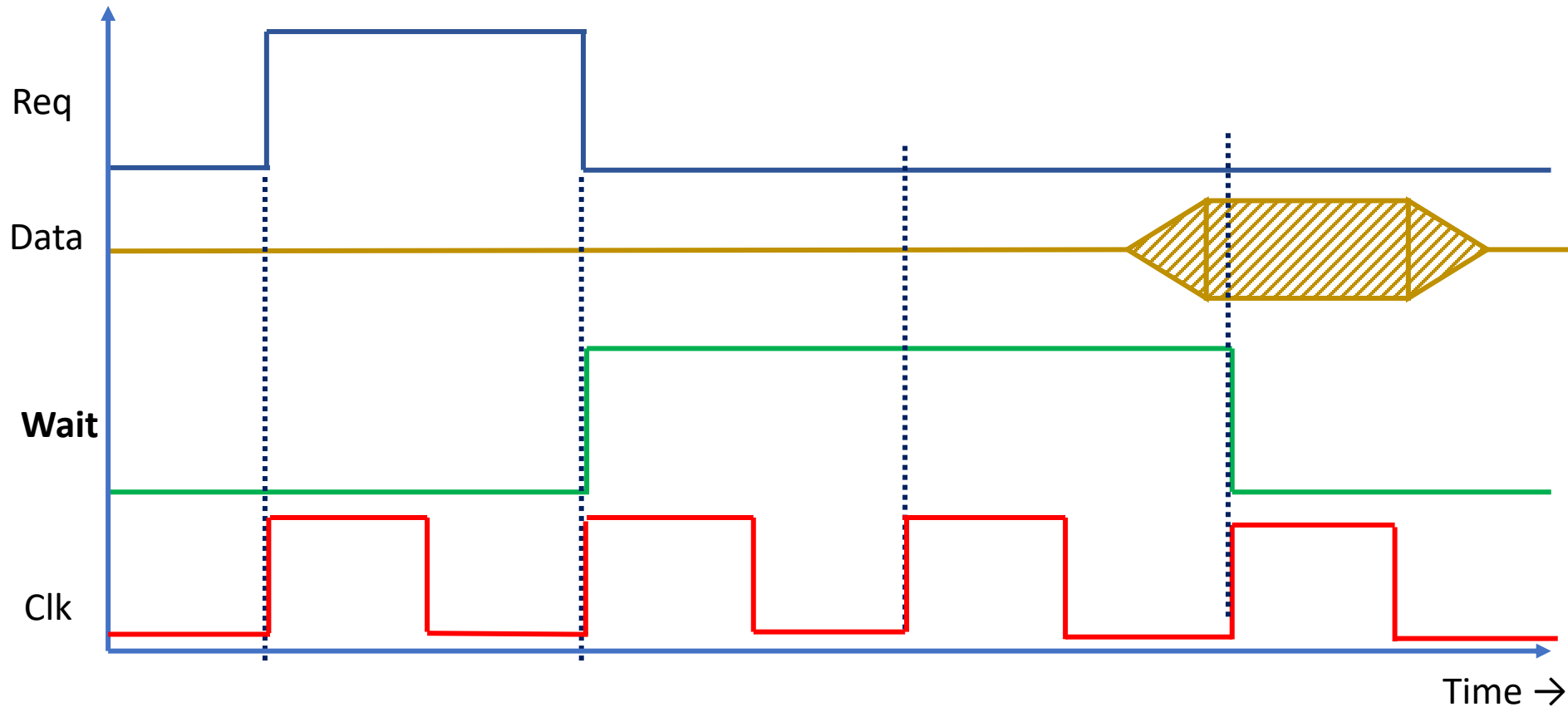


Slave can delay the Master by asserting Wait signal as it prepares the data and needs more clock cycles  
 When the slave un-asserts Wait signal, it acknowledges that data is now available for the Master to read  
 All interface signals are synchronized with Clock edge
 
# Four Cycle Asynchronous Signaling

RTZ – Return to Zero Signaling with No Clock



# Two Cycle Asynchronous Signaling

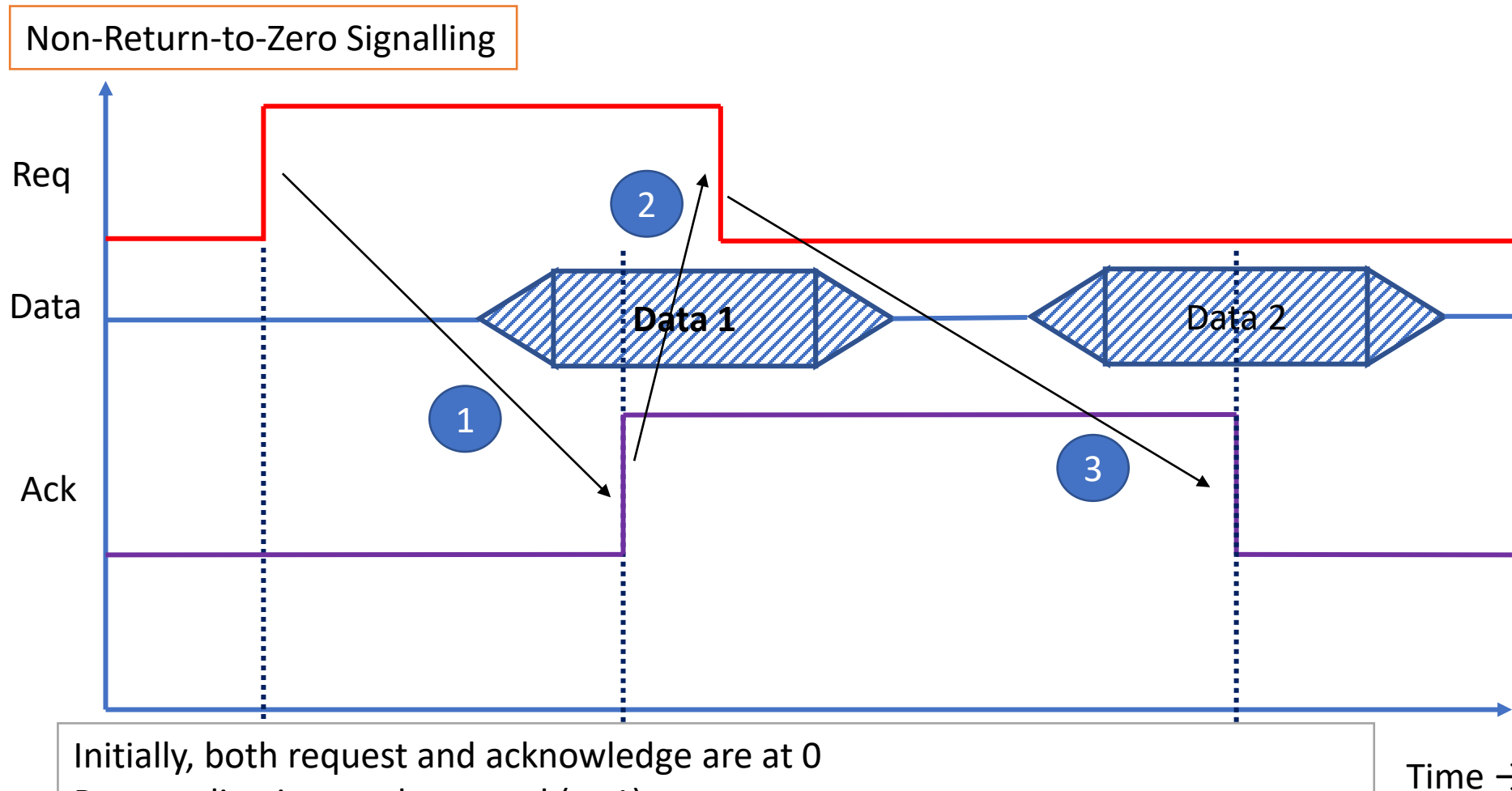

Initially, both request and acknowledge are at 0  
 Request line is complemented (to 1)  
 Slave notices change in Req, provides data, and complements the Ack line (to 1)  
 Further request and acknowledgement is by complementing the respective state

# Self-Timed Circuits

- A self-timed circuit can determine on its own when a request has been serviced by mimicking the worst-case propagation delay path by using special logic to delay the request signal.
- This guarantees sufficient time to compute the correct output.

