

Lecture 10

EE 421 / CS 425

Digital System Design


Fall 2023

Shahid Masud

Topics

- Metastability
- Synchronizers for capturing Asynchronous Inputs
- Signal Transfer with and without Clock
- Communication between modules in Complex Digital System
- Quiz 2 today

 
Objective – to reduce possible Metastability in capturing Asynchronous Input




Synchronizer Failure: When flipflop hangs in a Metastable State for a long time (indefinitely)

Normally, the flipflop output would settle to a stable 0 or 1 state after some time

Output Behaviour with Metastability

 

 **DFF is connected to produce metastability
As setup time is violated**



Oscilloscope trace of metastable behaviour


Eventually a stable state is reached

Problem occurs when flipflop is not stable within
One clock period

Synchronizers

- **Asynchronous inputs are problematic as their transitions are not predictable**
- **High speed digital circuits rely on synchronizers to create a time buffer for recovering from a metastable event; thus reducing the possibility that metastability will cause circuit to malfunction**
- **An asynchronous signal should be synchronized by one synchronizer only. If not, then multiple synchronized signals could be present in the system and one of these could be driven into metastable state**


Asynchronous Inputs to a Synchronous Digital System

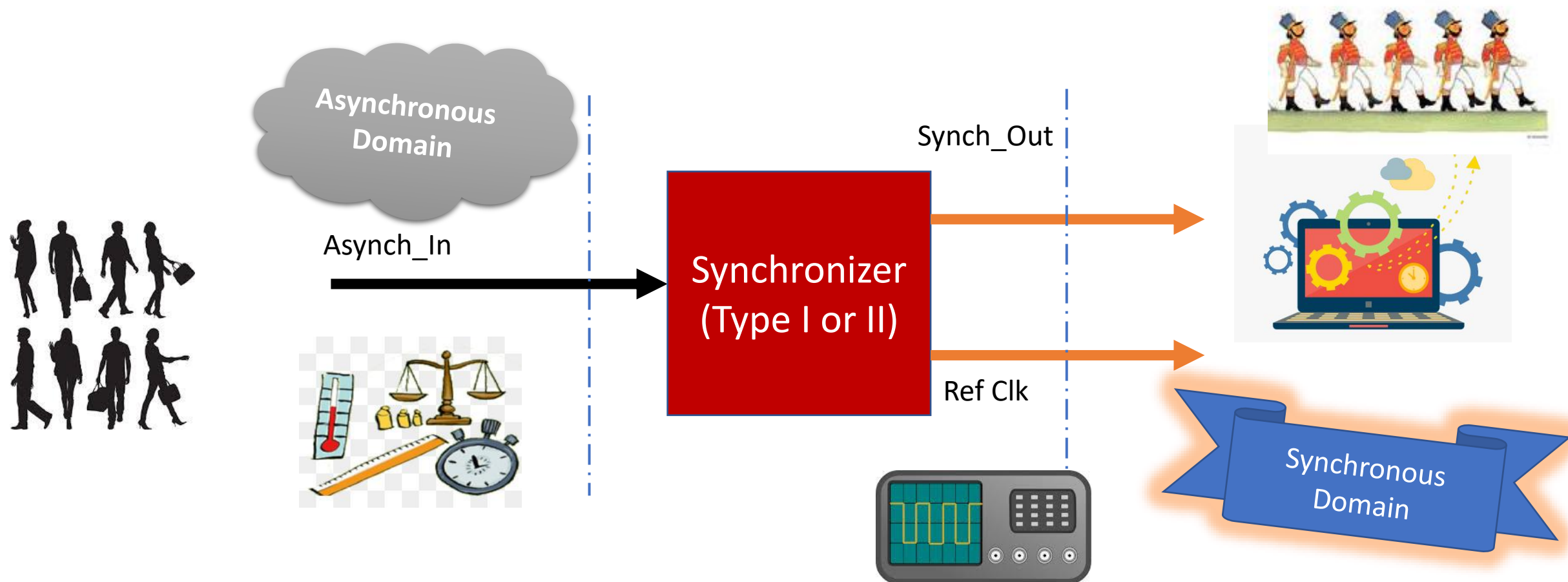

Synchronizer 1


Condition: The width of asynchronous input pulse is greater than period of the clock

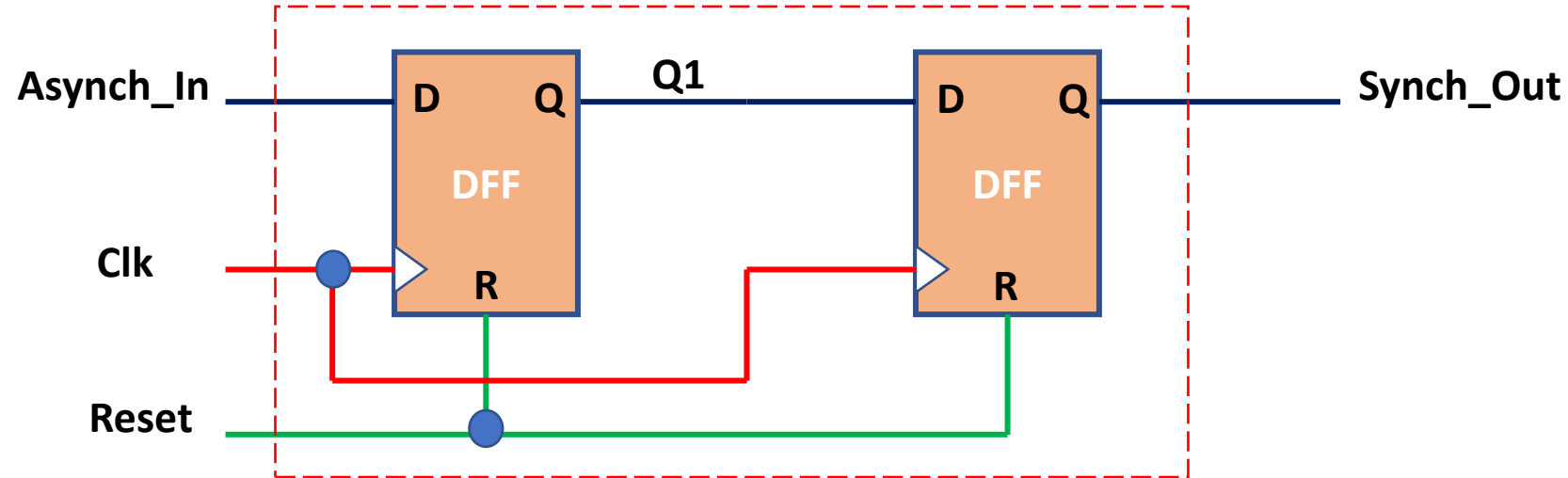Synchronizer is a multistage shift register




Reset Input 'R' is used as control to bring Synch_Out back to '0', as required

Timing Diagram – Synchronizer 1

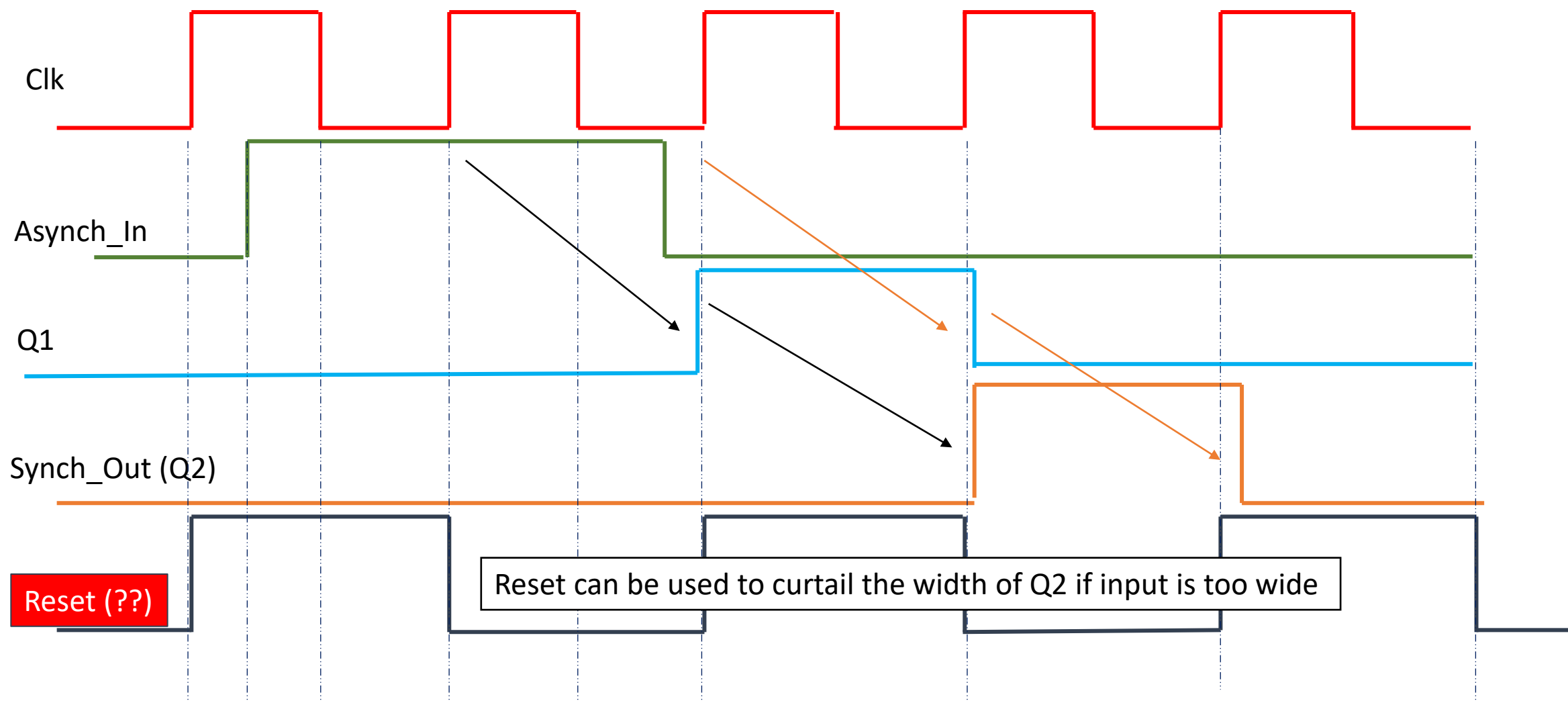


Synchronizer 2

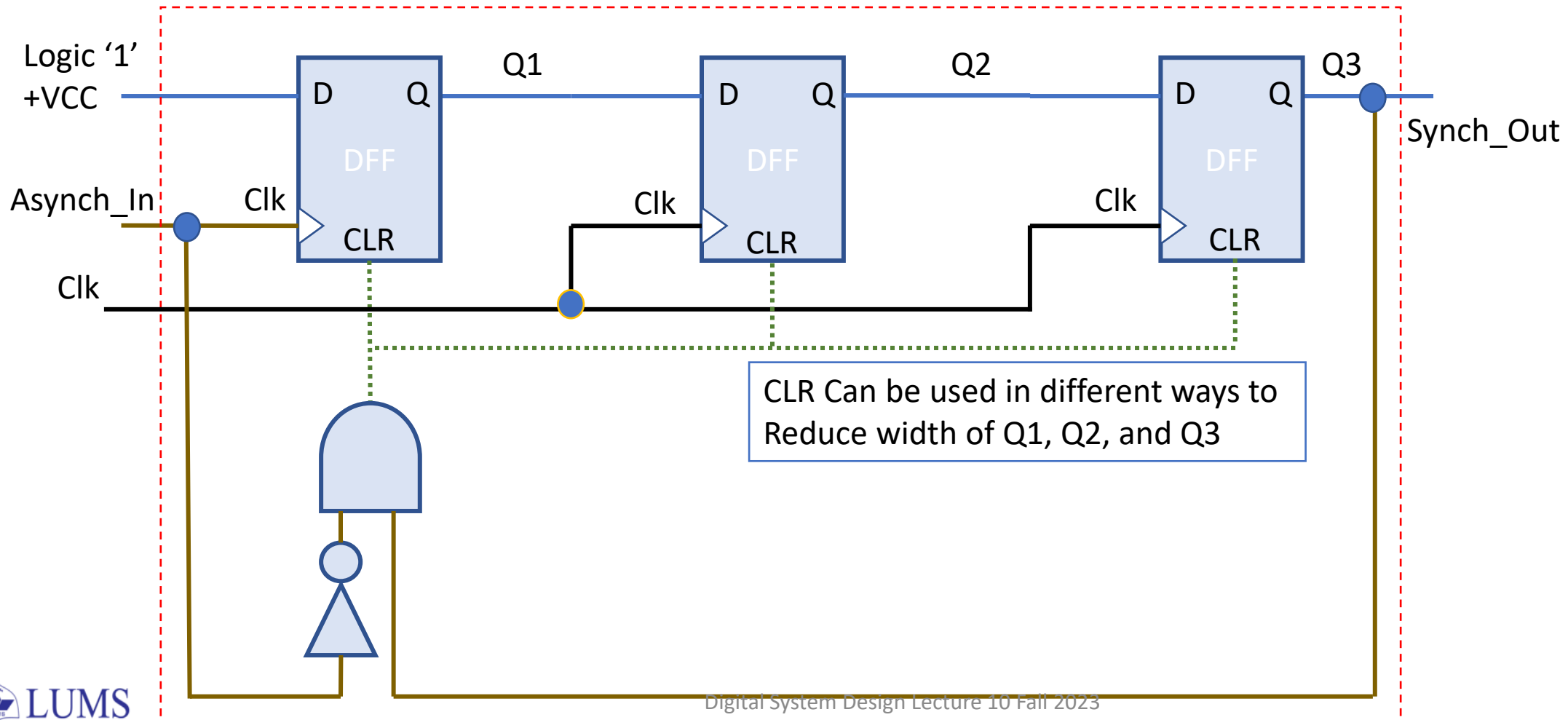Condition: Width of the asynchronous input pulse is less than the period of the clock



Timing Diagram – Synchronizer 2

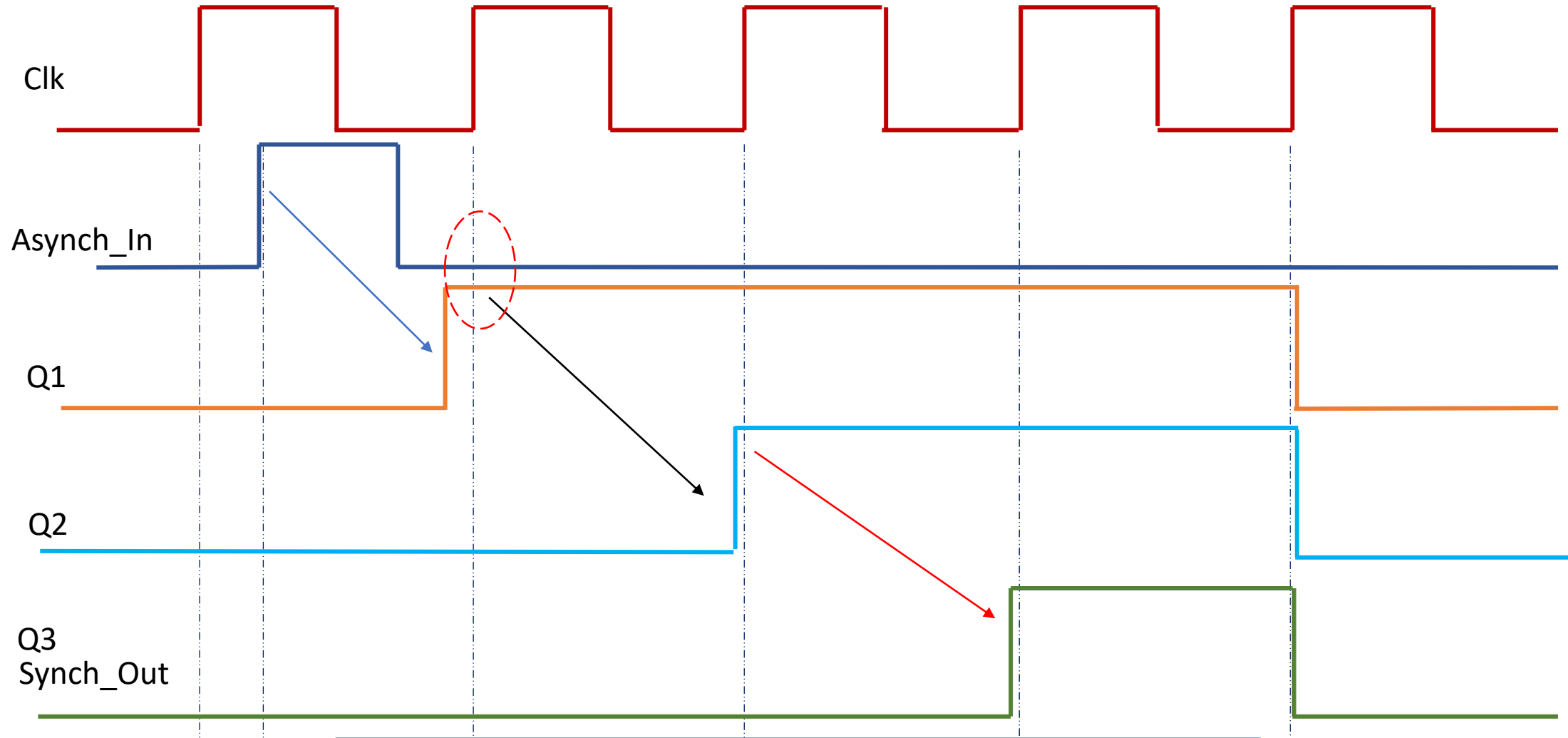


CLR input at DFF1 is used to bring back Q1 and then Q2 to Zero

Self-Timed and Speed Independent Circuits

- Having a completed Synchronous system is at times too challenging for a complex and fast digital system
- The limiting problem becomes how to distribute a single global clock without introducing intolerable clock skew
- The alternate is to partition the digital system into locally clocked pieces that communicate with each other using delay-insensitive signaling techniques (i.e. local clock for local communication)
- Each block proceeds at its own speed without the need for a global clock, synchronizing local communication whenever needed
- Usually a Request-Response Signalling method is employed

Data Reading across two Clock Domains

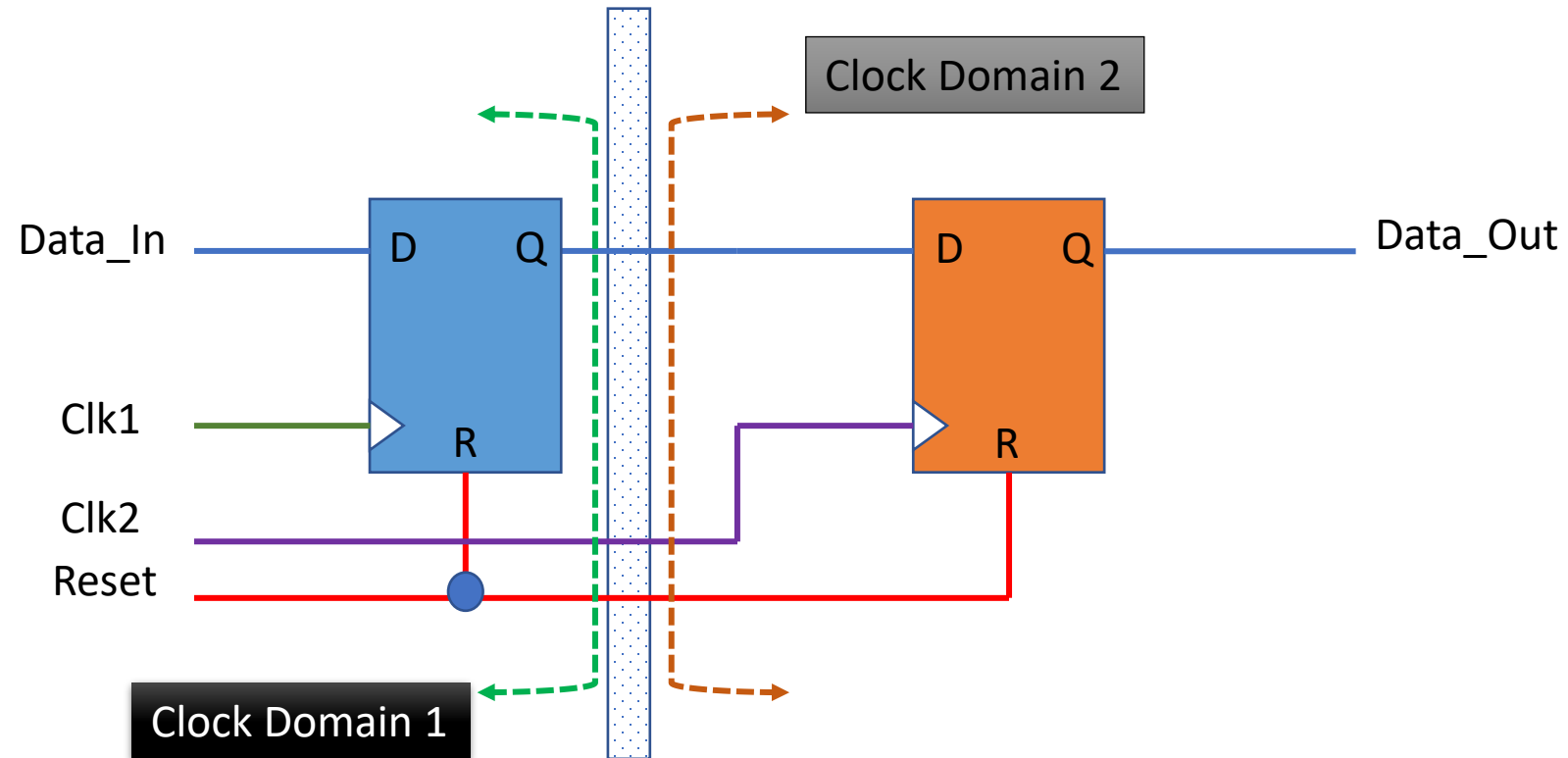

frequency of Clk1 is less than Clk2
 Otherwise, the **Synchronizer-2** is versatile and can be used here

Communication across modules in Complex SoC



- Communication Signaling across modules at different clock speeds
- Self-timed circuits

Self-Timed and Speed Independent Circuits


- Having a completed Synchronous system is at times too challenging for a complex and fast digital system
- The limiting problem becomes how to distribute a single global clock without introducing intolerable clock skew
- The alternate is to partition the digital system into locally clocked pieces that communicate with each other using delay-insensitive signaling techniques (i.e. local clock for local communication)
- Each block proceeds at its own speed without the need for a global clock, synchronizing local communication whenever needed
- Usually a Request-Response Signaling method is employed

Request / Acknowledge Signaling

Independently clocked Subsystems

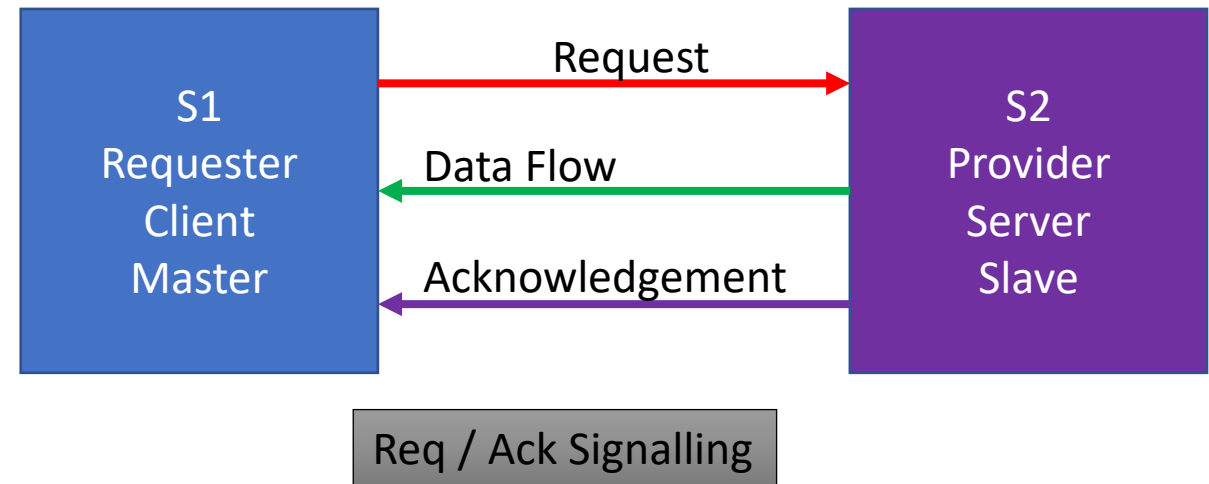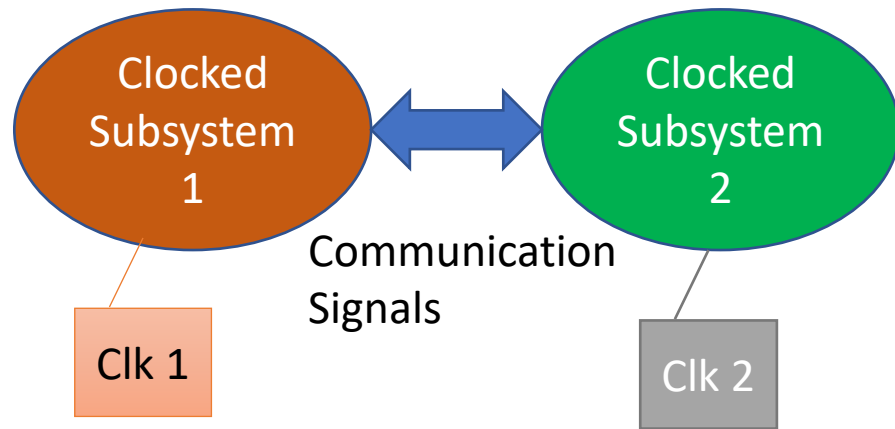


Synchronous Req / Ack Signaling

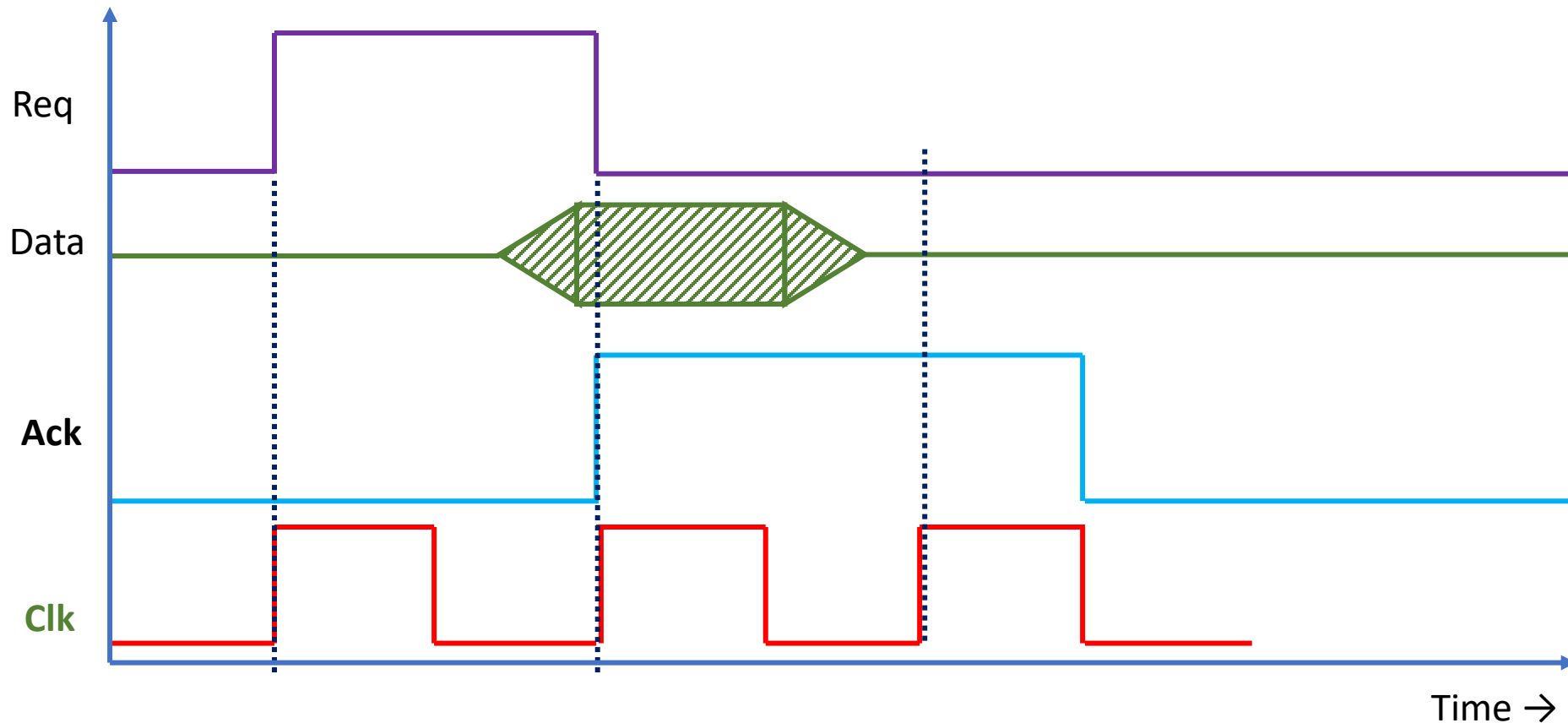

Req and Ack signals are synchronized to **Clk**


Synchronous Req with Wait Signaling

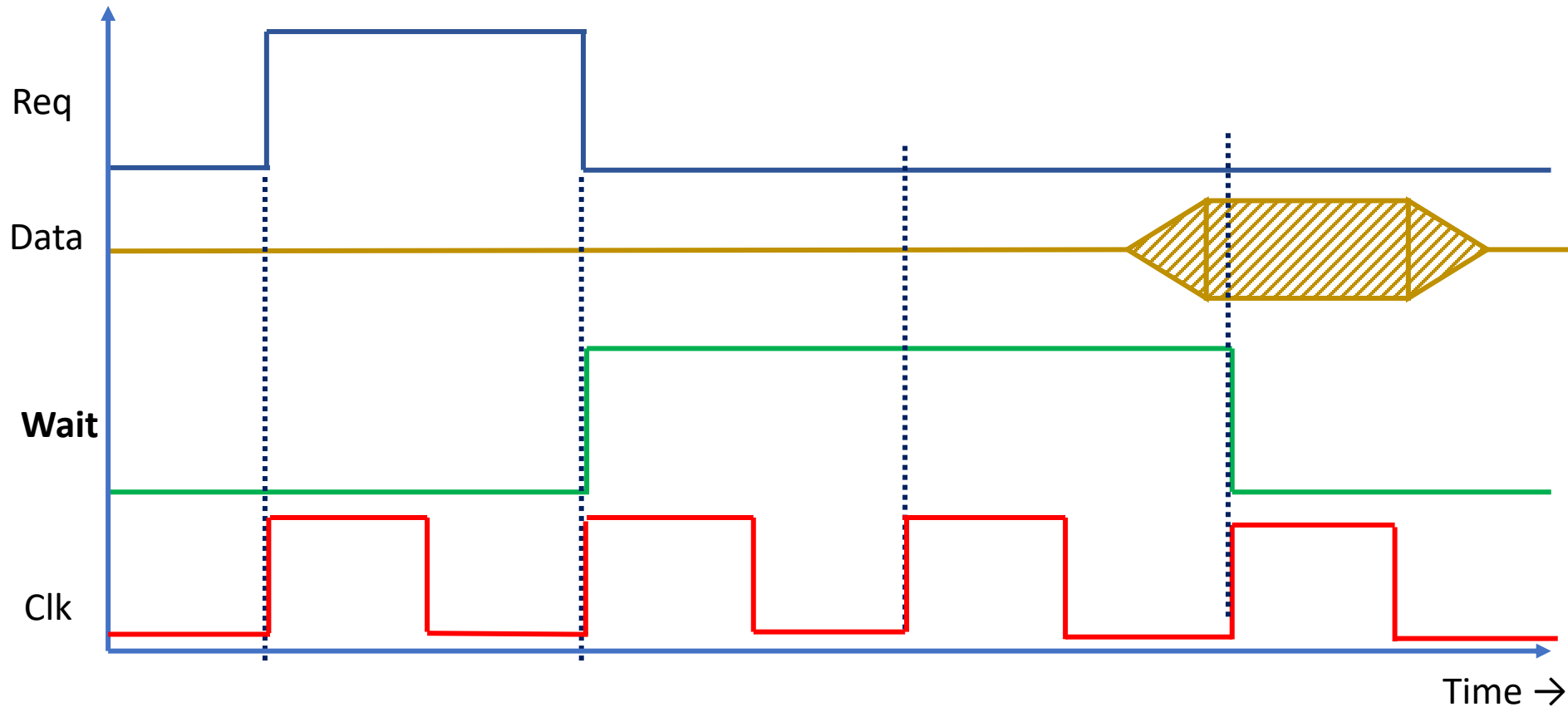

Slave can delay the Master by asserting Wait signal as it prepares the data and needs more clock cycles
 When the slave un-asserts Wait signal, it acknowledges that data is now available for the Master to read
 All interface signals are synchronized with Clock edge


Four Cycle Asynchronous Signaling

 RTZ – Return to Zero Signaling with No Clock



Two Cycle Asynchronous Signaling

Non-Return-to-Zero Signalling

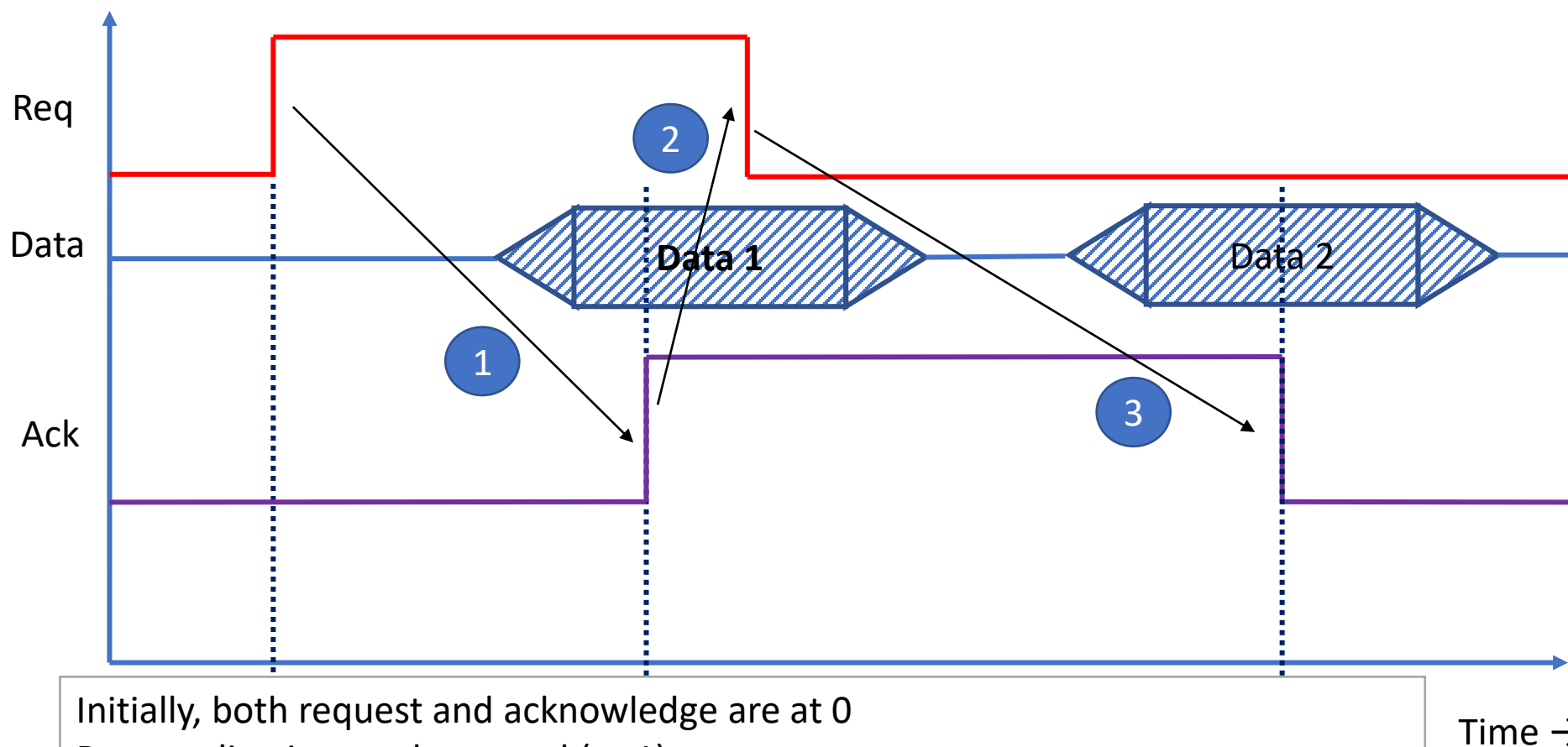

Initially, both request and acknowledge are at 0
 Request line is complemented (to 1)
 Slave notices change in Req, provides data, and complements the Ack line (to 1)
 Further request and acknowledgement is by complementing the respective state

Self-Timed Circuits

- A self-timed circuit can determine on its own when a request has been serviced by mimicking the worst-case propagation delay path by using special logic to delay the request signal.
- This guarantees sufficient time to compute the correct output.

