

# Lecture 7

## EE 421 / CS 425

# Digital System Design

Spring 2023

Shahid Masud

# Topics


- Three State Drivers (or Buffers)
- D and T Flipflops
- Some Examples of DFF based Circuits:
  - Shift Registers
  - Counters
- Analyzing DFF based Circuits
- Synthesizing DFF Based Counters or Sequencers

Remember:  
Quiz 2 Next Week


# Three State Buffers for Processor Buses

- Buses are multi-wire signal paths that connect multiple functional units in a computer system, e.g., Address bus, peripheral bus, etc.
- Simplifies design and architecture of a computer system
- Tradeoff is that the access to the bus has to be managed to avoid conflicts
- Three state hardware devices provide a dynamic interface between a bus and a circuit, providing signals when enabled else an open circuit
- The input goes to the output of the tri-state buffer when enable signal is asserted


# Three State Bus Drivers

 

| x | en | y    |
|---|----|------|
| 0 | 0  | Hi_Z |
| 0 | 1  | 0    |
| 1 | 0  | Hi_Z |
| 1 | 1  | 1    |

 

| x | en | y    |
|---|----|------|
| 0 | 0  | 0    |
| 0 | 1  | Hi_Z |
| 1 | 0  | 1    |
| 1 | 1  | Hi_Z |

 


Typical Bus Structure utilizing 3-state buffers




**Inverting and Non-Inverting 3-State Buffers / Drivers Exist**

**The Enable can be active high or active low**

 **Buffers with Hysteresis Loop are available for better noise immunity**



# D Flipflops – Behaviour and Equation

   



## Characteristic Equation:

$$Q(t+1) = D$$

Q after clock pulse gets value of D

| D | Q(t+1)   |
|---|----------|
| 0 | 0; Reset |
| 1 | 1; Set   |

# T Flipflop – Behaviour and Equation

 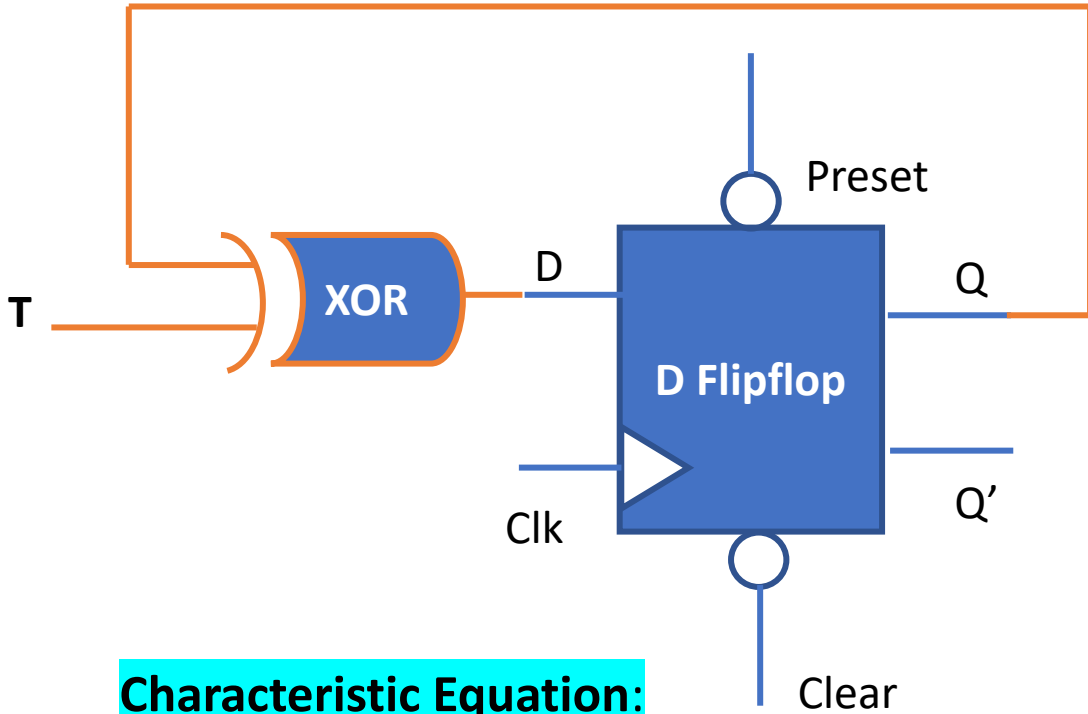


## Characteristic Equation:

$$Q(t+1) = T \oplus Q$$

$$= T'Q + TQ'$$

| T | Q(t+1)                      |
|---|-----------------------------|
| 0 | Q(t); No change             |
| 1 | Q'(t); Toggle or Complement |

 

**In this course,**

**We will mostly use D Flipflops  
and sometimes T Flipflops**



**We want to study complex and high speed designs**

# Sequential Circuits: Counters, Sequencers, State Machines

- **Counters:** count in a fixed sequence, up or down
- **Sequencers:** sequence through a pre-defined arbitrary sequence
- **State Machines:** Sequential and Combinational Circuits work together to go one of many next states based on current inputs




# Moving Through Register Chain

 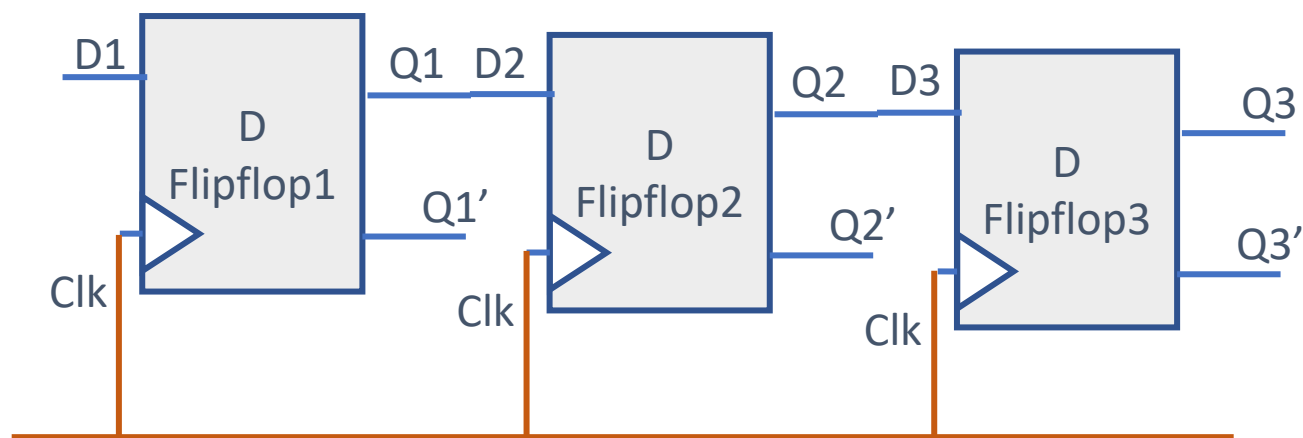
 
# 3 DFF Shift Register Timing Diagram from a website


Look closely at the Area close to Clock transition, Shaded pink lines



We assume that there is a small delay at Q state of each flipflop to make the timing diagram easily understandable.

But in reality, the situation would be a little more complicated than this simple time delay.
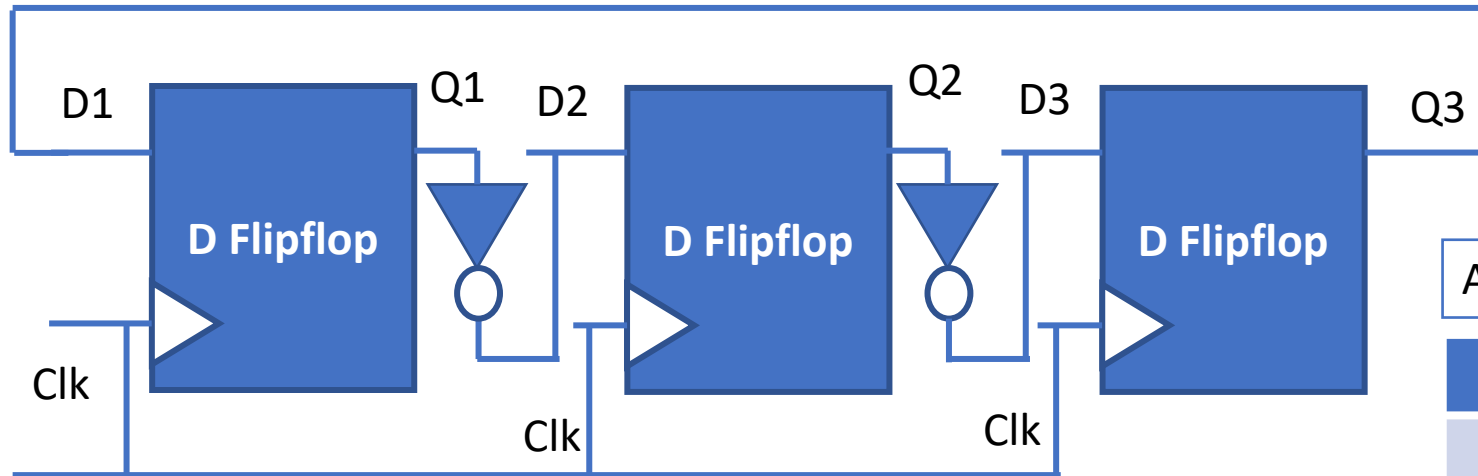
# Cyclic Shift Register using D flipflops



Assume all DFFs are Cleared to **0** at Startup

| Clock No. | Q1   | Q2   | Q3   |
|-----------|------|------|------|
| 1         | 0    | 0    | 0    |
| 2         | 0    | 1    | 1    |
| 3         | 1    | 1    | 0    |
| 4         | 0    | 0    | 0    |
| 5         | 0    | 1    | 1    |
| 6         | 1    | 1    | 0    |
| 7         | 0    | 0    | 0    |
| CONTINUE  | .... | .... | .... |


After the clock edge:

$Q1(t+1)$  becomes same as  $Q3(t)$

$Q2(t+1)$  becomes inverse of  $Q1(t)$

$Q3(t+1)$  becomes inverse of  $Q2(t)$

# Tail Ring Counter Four Stage

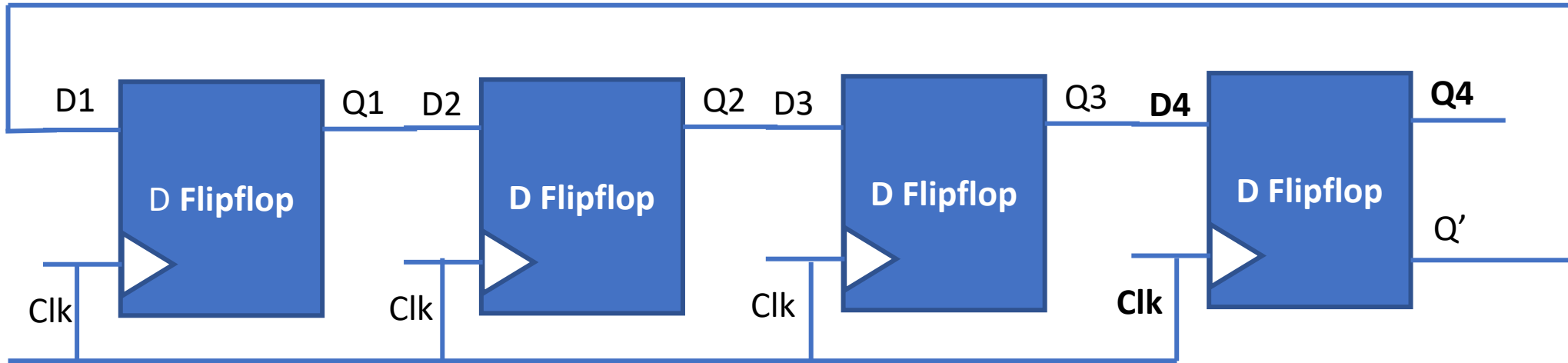


State  
Transition  
Table

| Sequence No. | Q1 | Q2 | Q3 | Q4 |
|--------------|----|----|----|----|
| 1            | 0  | 0  | 0  | 0  |
| 2            | 1  | 0  | 0  | 0  |
| 3            | 1  | 1  | 0  | 0  |
| 4            | 1  | 1  | 1  | 0  |
| 5            | 1  | 1  | 1  | 1  |
| 6            | 0  | 1  | 1  | 1  |
| 7            | 0  | 0  | 1  | 1  |
| 8            | 0  | 0  | 0  | 1  |
| 9            | 0  | 0  | 0  | 0  |

# Analyze Sequential Circuits

- Concept of State Equations
- Concept of State Tables
- Logic Steering through Combinational Logic
- Arbitrary Counting and Sequencing
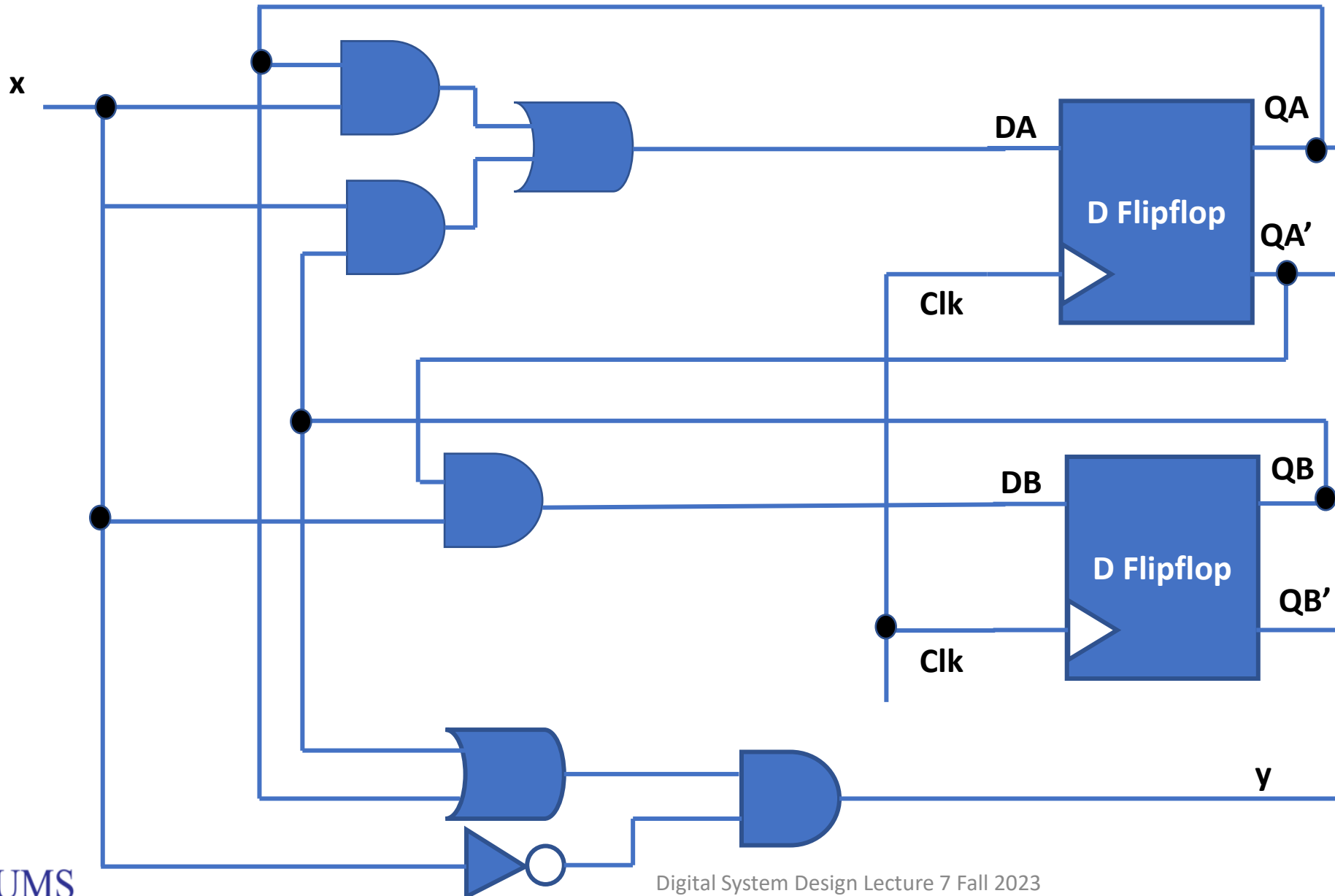
# Example Sequential Circuit for Analysis



# Determine State Equations

$$QA(t+1) = QA(t)x(t) + QB(t) x(t)$$

$$QB(t+1) = QA'(t) x(t)$$

$$y(t) = [QA(t) + QB(t)]x'(t)$$



Can be written in a simplified way:

$$QA(t+1) = QA.(x) + QB.(x)$$

$$QB(t+1) = QA'.(x)$$

$$y = (QA + QB).(x')$$

# Determine State Table from State Equations


| Present State | Present State | Input | Next State | Next State | Output |
|---------------|---------------|-------|------------|------------|--------|
| QA(t)         | QB(t)         | x     | QA(t+1)    | QB(t+1)    | y      |
| 0             | 0             | 0     | 0          | 0          | 0      |
| 0             | 0             | 1     | 0          | 1          | 0      |
| 0             | 1             | 0     | 0          | 0          | 1      |
| 0             | 1             | 1     | 1          | 1          | 0      |
| 1             | 0             | 0     | 0          | 0          | 1      |
| 1             | 0             | 1     | 1          | 0          | 0      |
| 1             | 1             | 0     | 0          | 0          | 1      |
| 1             | 1             | 1     | 1          | 0          | 0      |



# Compact State Table

| Present State |        | Next State   |          |              |          | Output  |         |
|---------------|--------|--------------|----------|--------------|----------|---------|---------|
|               |        | When $x = 0$ |          | When $x = 1$ |          | $x = 0$ | $x = 1$ |
| $A(t)$        | $B(t)$ | $A(t+1)$     | $B(t+1)$ | $A(t+1)$     | $B(t+1)$ | $y$     | $y$     |
| 0             | 0      | 0            | 0        | 0            | 1        | 0       | 0       |
| 0             | 1      | 0            | 0        | 1            | 1        | 1       | 0       |
| 1             | 0      | 0            | 0        | 1            | 0        | 1       | 0       |
| 1             | 1      | 0            | 0        | 1            | 0        | 1       | 0       |
 
# Using Memory to design an arbitrary sequencer



**Desired Sequence is  
Stored in Memory Locations**

# Design of Synchronous Counter using DFF

- Express each number of sequence in binary code
- Use appropriate number of DFFs to represent entire sequence
- Make a State Table representing Present State and Next State
- Determine Excitation Logic Expression for Next States using K-Maps
- Complete the DFF Based Circuit using Excitation Expressions

# Example Design of a Synchronous Counter (Sequencer)

Make a Synchronous Counter for sequence {0 → 3 → 6 → 9 → 12 → 0}

**Step 1: Describe Behavior Through Truth Table**

Desired Sequence In Binary form:

| Clock No. | Sequence | Binary |    |    |    |
|-----------|----------|--------|----|----|----|
|           |          | Q3     | Q2 | Q1 | Q0 |
| 1         | 0        | 0      | 0  | 0  | 0  |
| 2         | 3        | 0      | 0  | 1  | 1  |
| 3         | 6        | 0      | 1  | 1  | 0  |
| 4         | 9        | 1      | 0  | 0  | 1  |
| 5         | 12       | 1      | 1  | 0  | 0  |
| 6         | 0        | 0      | 0  | 0  | 0  |



# Present State – Next State Table

| Clock No. | Sequence | Present State |       |       |       | Next State |         |         |         |
|-----------|----------|---------------|-------|-------|-------|------------|---------|---------|---------|
|           |          | Q3(t)         | Q2(t) | Q1(t) | Q0(t) | Q3(t+1)    | Q2(t+1) | Q1(t+1) | Q0(t+1) |
| 1         | 0        | 0             | 0     | 0     | 0     | 0          | 0       | 1       | 1       |
| 2         | 3        | 0             | 0     | 1     | 1     | 0          | 1       | 1       | 0       |
| 3         | 6        | 0             | 1     | 1     | 0     | 1          | 0       | 0       | 1       |
| 4         | 9        | 1             | 0     | 0     | 1     | 1          | 1       | 0       | 0       |
| 5         | 12       | 1             | 1     | 0     | 0     | 0          | 0       | 0       | 0       |
| 6         | 0        | 0             | 0     | 0     | 0     | 0          | 0       | 1       | 1       |

**DFF make it convenient as Present State to Next State is only separated by a Clock Pulse**

# Make K-Maps to determine Next State using Next State Outputs as K-Map Entries


K-Map for D0 (Input that will give correct next state)

| Q3Q2, Q1Q0 | 00 | 01 | 11 | 10 |
|------------|----|----|----|----|
| 00         | 1  |    | 0  |    |
| 01         |    |    |    | 1  |
| 11         | 0  |    |    |    |
| 10         |    | 0  |    |    |

State Equation:

$$D0 = Q3'Q2'Q1'Q0' + Q3'Q2Q1Q0'$$

# K-Map for D1

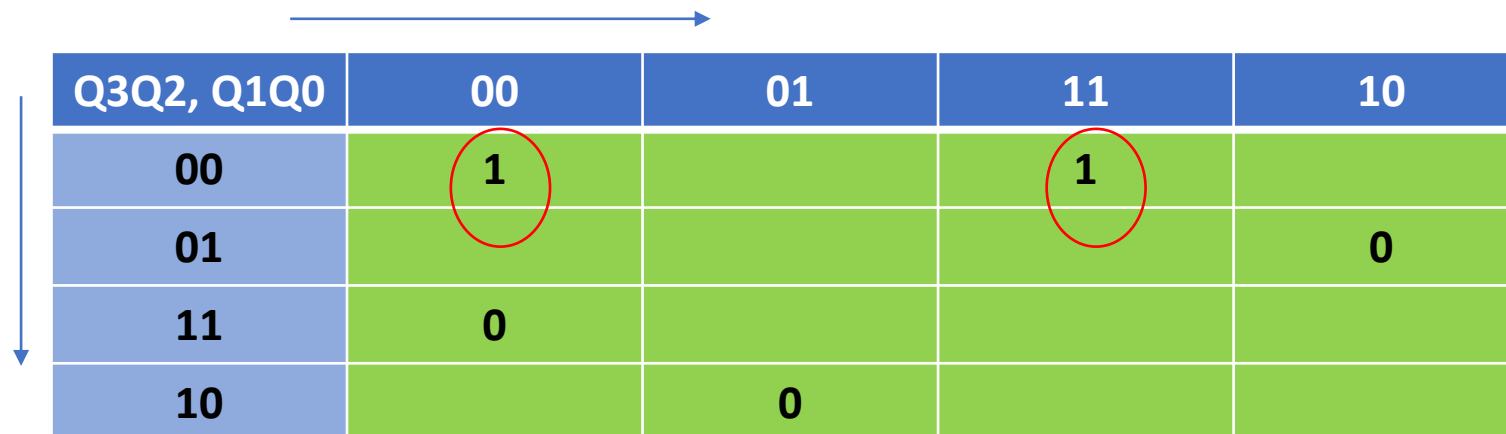


A Karnaugh Map for the output D1. The map is a 4x4 grid. The columns are labeled with Q3Q2, Q1Q0 values: 00, 01, 11, and 10. The rows are labeled with Q3Q2, Q1Q0 values: 00, 01, 11, and 10. The cells contain the values of D1 for each combination of inputs. The cells (00, 00) and (11, 00) contain the value 1 and are circled in red. The cell (01, 01) contains the value 0. The cell (10, 01) contains the value 0. All other cells are empty.

| Q3Q2, Q1Q0 | 00 | 01 | 11 | 10 |
|------------|----|----|----|----|
| 00         | 1  |    | 1  |    |
| 01         |    |    |    | 0  |
| 11         | 0  |    |    |    |
| 10         |    | 0  |    |    |

State Equation:

$$D1 = Q3'Q2'Q1'Q0' + Q3'Q2'Q1Q0$$

# K-Map for D2

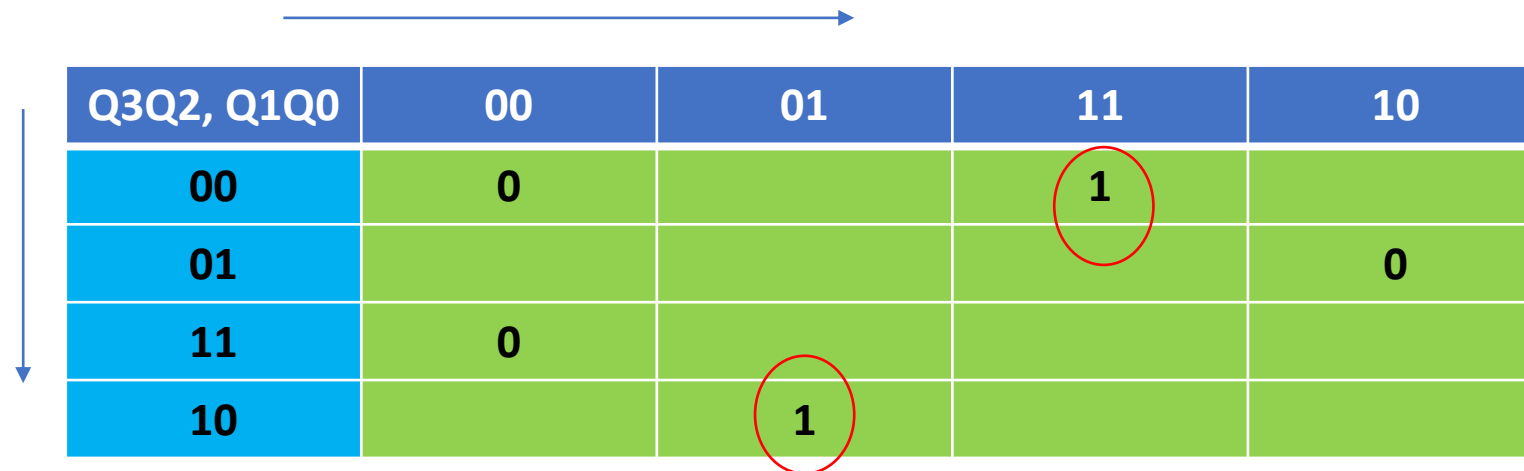

| Q3Q2, Q1Q0 | 00 | 01 | 11 | 10 |
|------------|----|----|----|----|
| 00         | 0  |    | 1  |    |
| 01         |    |    |    | 0  |
| 11         | 0  |    |    |    |
| 10         |    | 1  |    |    |

State Equation:

$$D2 = Q3Q2'Q1'Q0 + Q3'Q2'Q1Q0$$




# K-Map for D3

| Q3Q2, Q1Q0 | 00 | 01 | 11 | 10 |
|------------|----|----|----|----|
| 00         | 0  |    | 0  |    |
| 01         |    |    |    | 1  |
| 11         | 0  |    |    |    |
| 10         |    | 1  |    |    |

State Equation:

$$D3 = Q3'Q2Q1Q0' + Q3Q2'Q1'Q0$$

# Final Circuit Design of Sequencer

 

**Similar circuit for  
Other inputs D1 to D3  
to implement State Equations**

**For example, state equations:**

$$D0 = Q3'Q2'Q1'Q0' + Q3'Q2Q1Q0'$$

$$D1 = Q3'Q2'Q1'Q0' + Q3'Q2'Q1Q0$$

$$D2 = Q3Q2'Q1'Q0 + Q3'Q2'Q1Q0$$

$$D3 = Q3'Q2Q1Q0' + Q3Q2'Q1'Q0$$

