


Outline

- A simple implementation: Single Cycle
 - Data path and control
- Design Strategy
- Control Path Implementation
- Performance considerations


MIPS subset for implementation

- Arithmetic - logic instructions
 - add, sub, and, or, slt
- Memory reference instructions
 - lw, sw
- Control flow instructions
 - beq, j

Design overview

 

Division into data path and control

 


Datapath for add,sub,and,or,slt

- fetch instruction
 - address the register file
 - pass operands to ALU
 - pass result to register file
 - increment PC
- actions required


Format: add \$t0, \$s1, \$s2

000000	10001	10010	01000	00000	100000
op	rs	rt	rd	shamt	funct


Fetching instruction

 


Addressing RF

 


Passing operands to ALU

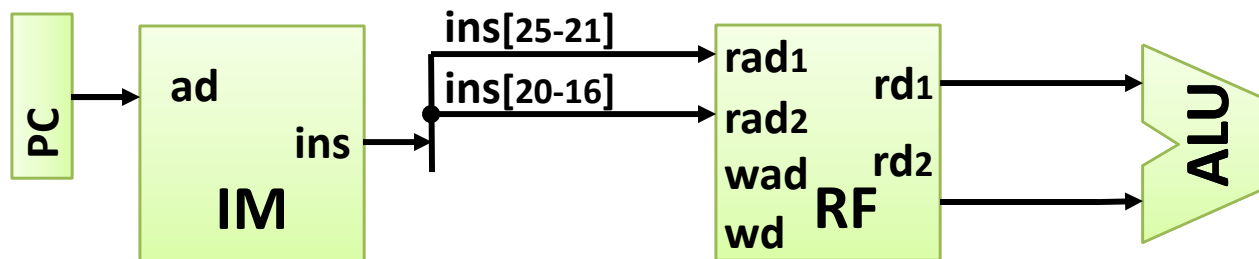

Passing the result to RF

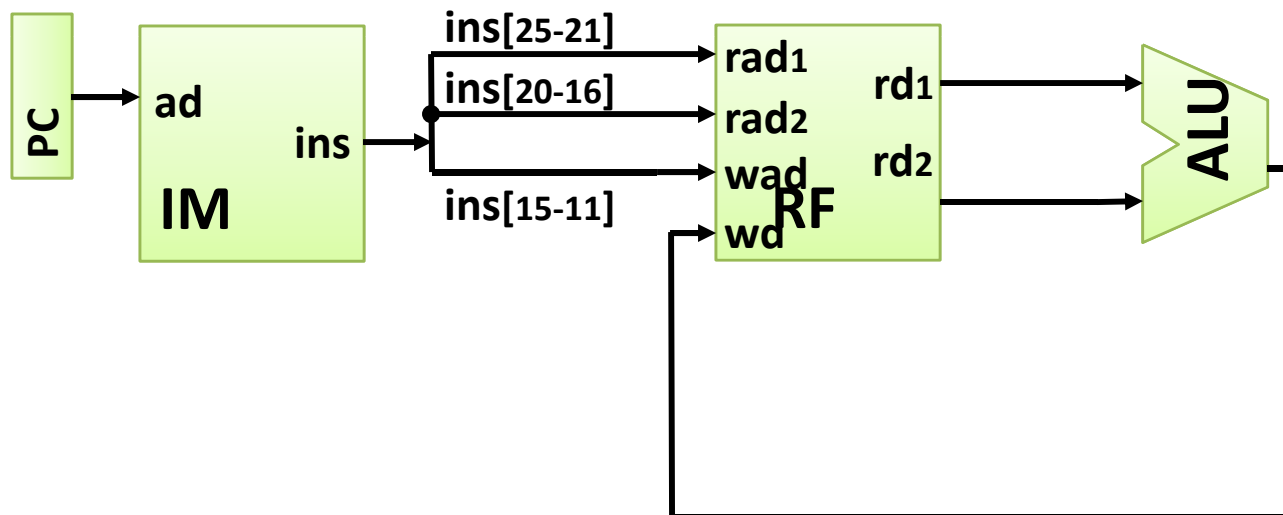

Incrementing PC

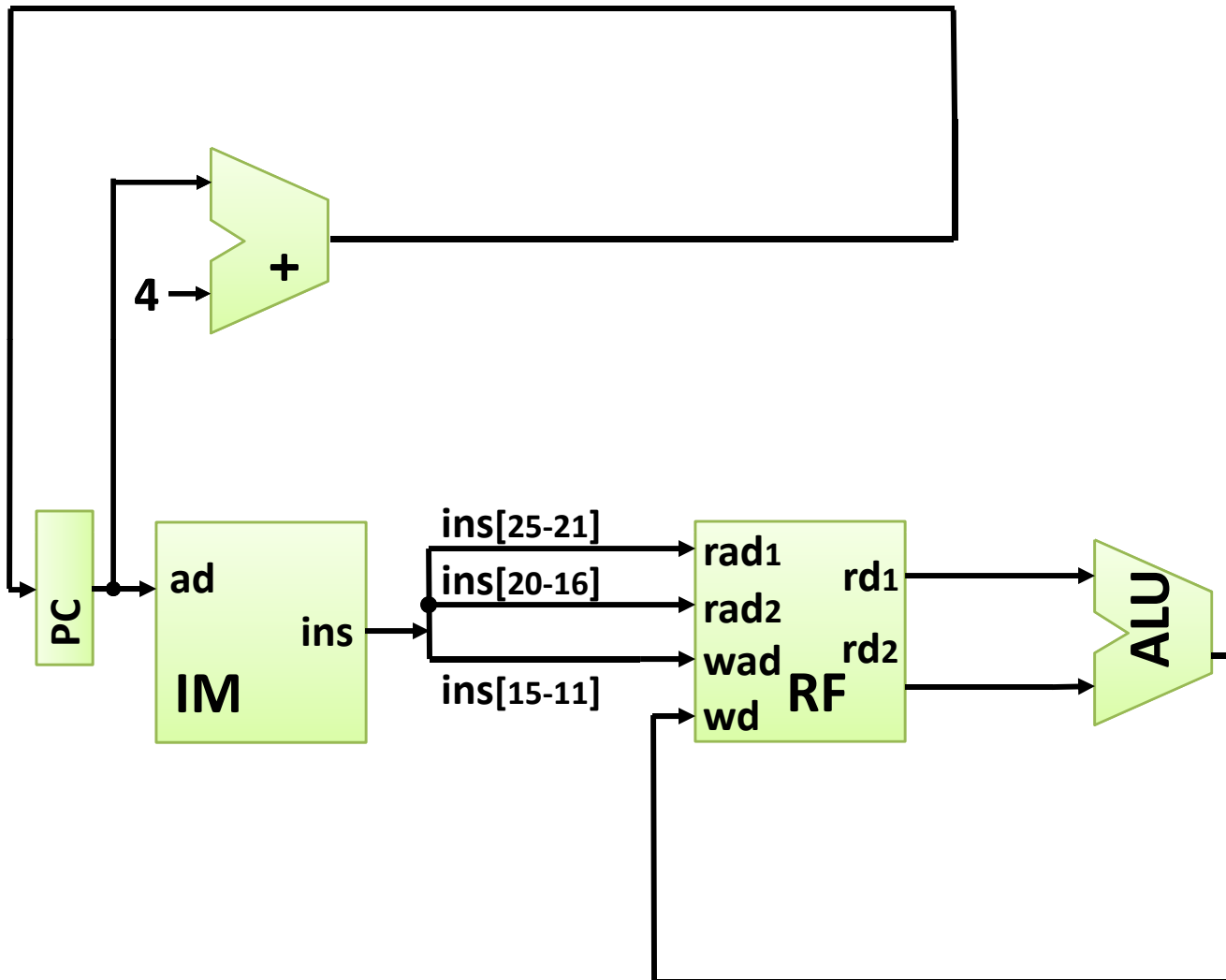


Load and Store instructions


- format : I
- Example: lw \$t0, 32(\$s2)

35	18	9	32
op	rs	rt	16 bit number

Adding “sw” instruction

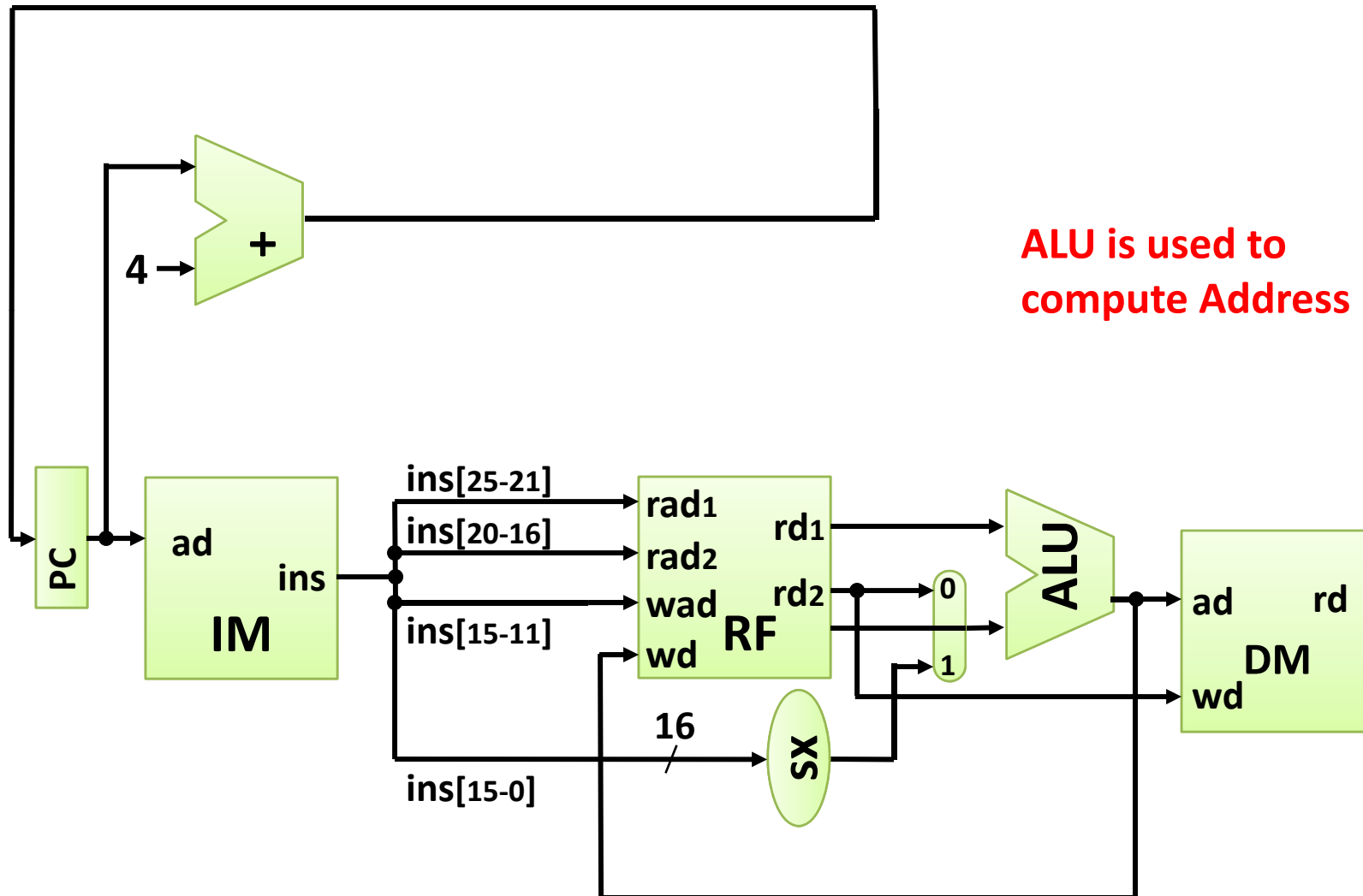

Adding “lw” instruction

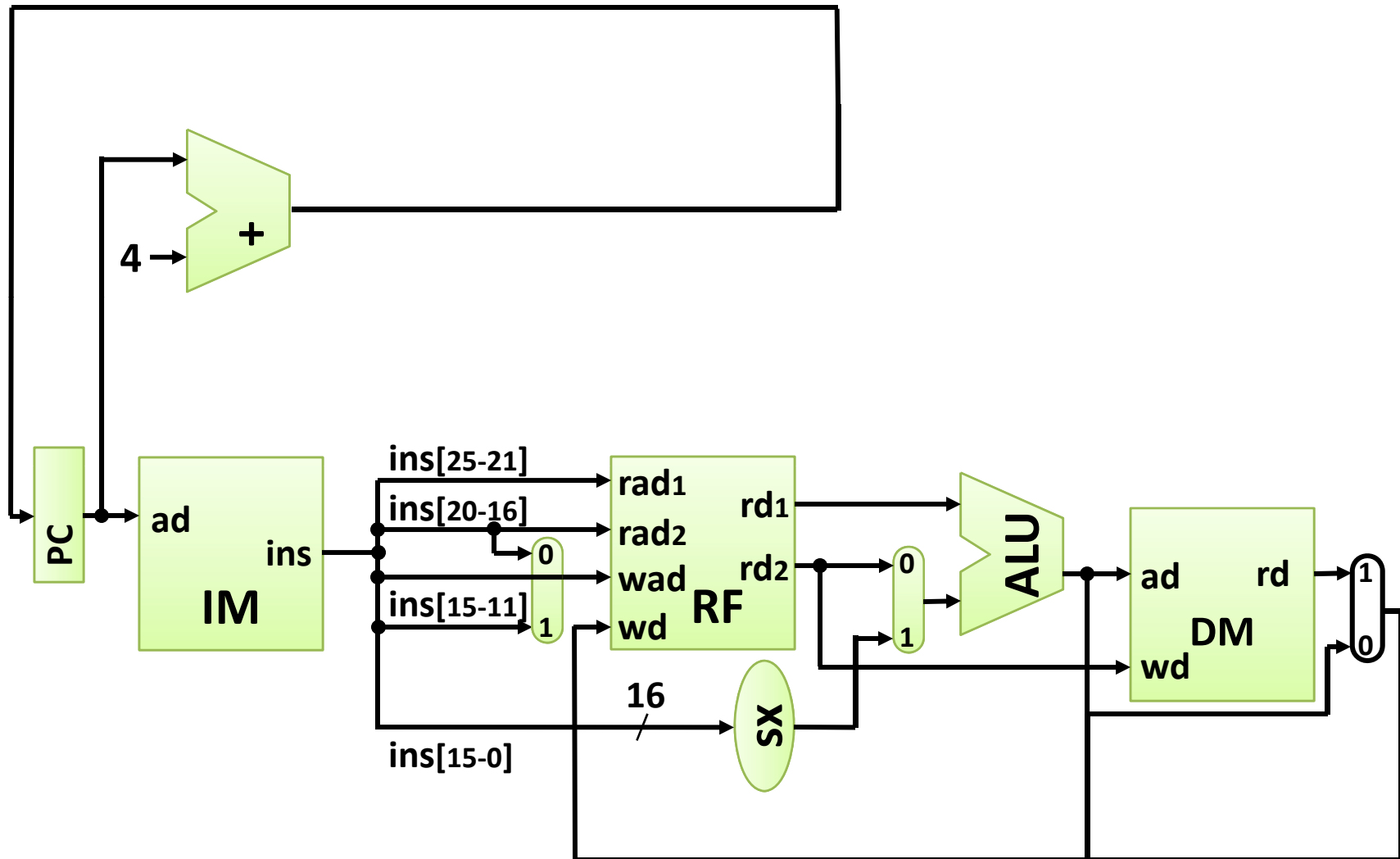


Format of beq instruction





- beq I - format

op	rs	rt	16 bit number
----	----	----	---------------

Adding “beq” instruction

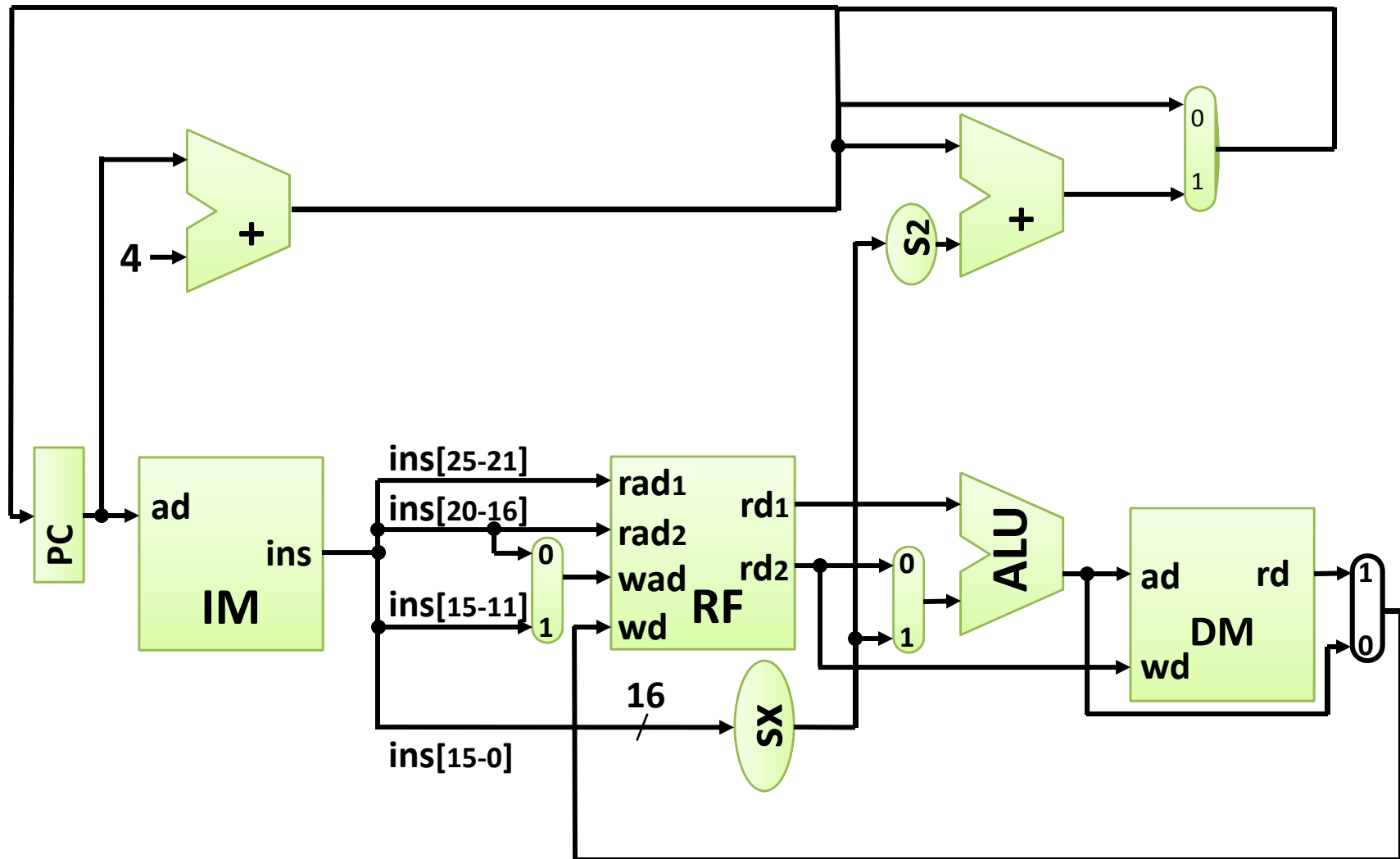

    MIPS components - bit manipulation circuits




Format of jump instruction


- j J - format

op	26 bit number
----	---------------


Adding “j” instruction

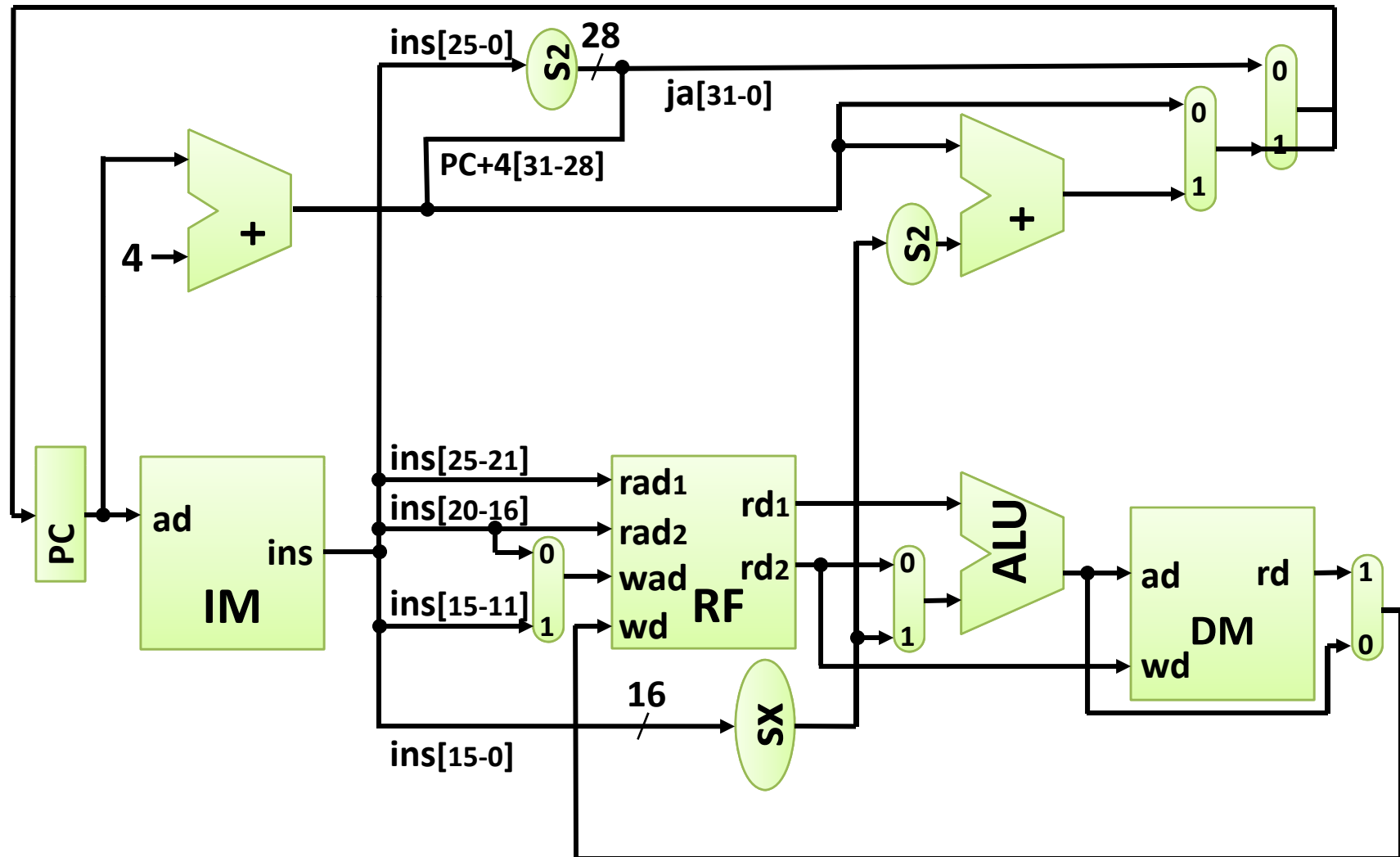

Control signals

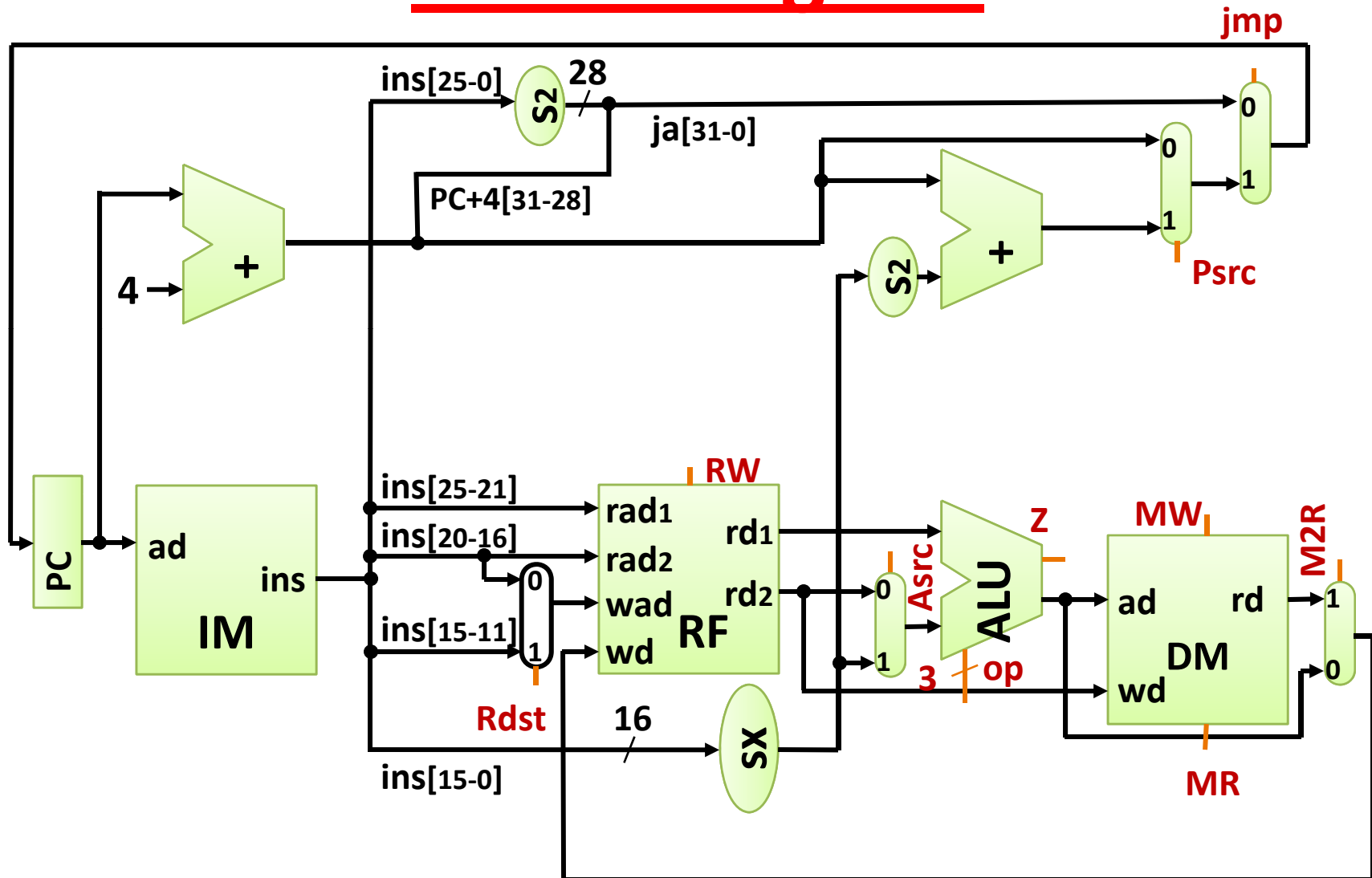


Datapath + Control

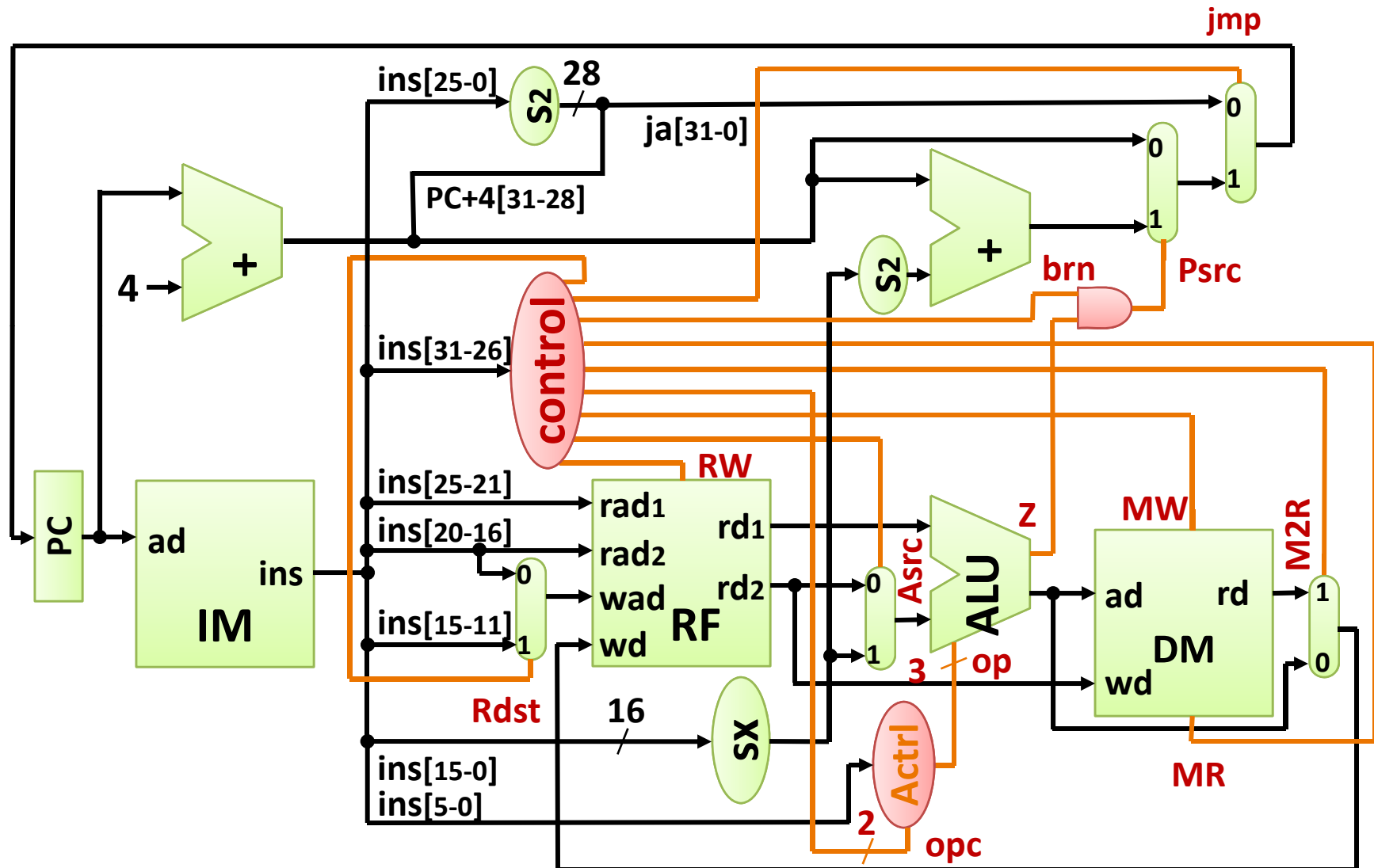


Analyzing performance

Components	Delay
Register	0
Adder	t_+
ALU	t_A
MUX	0
RF	t_R
Instruction Memory	t_I
Data Memory	t_m
Bit manipulation	0


Delay for {add, sub, and, or, slt}

 


Delay for {sw}

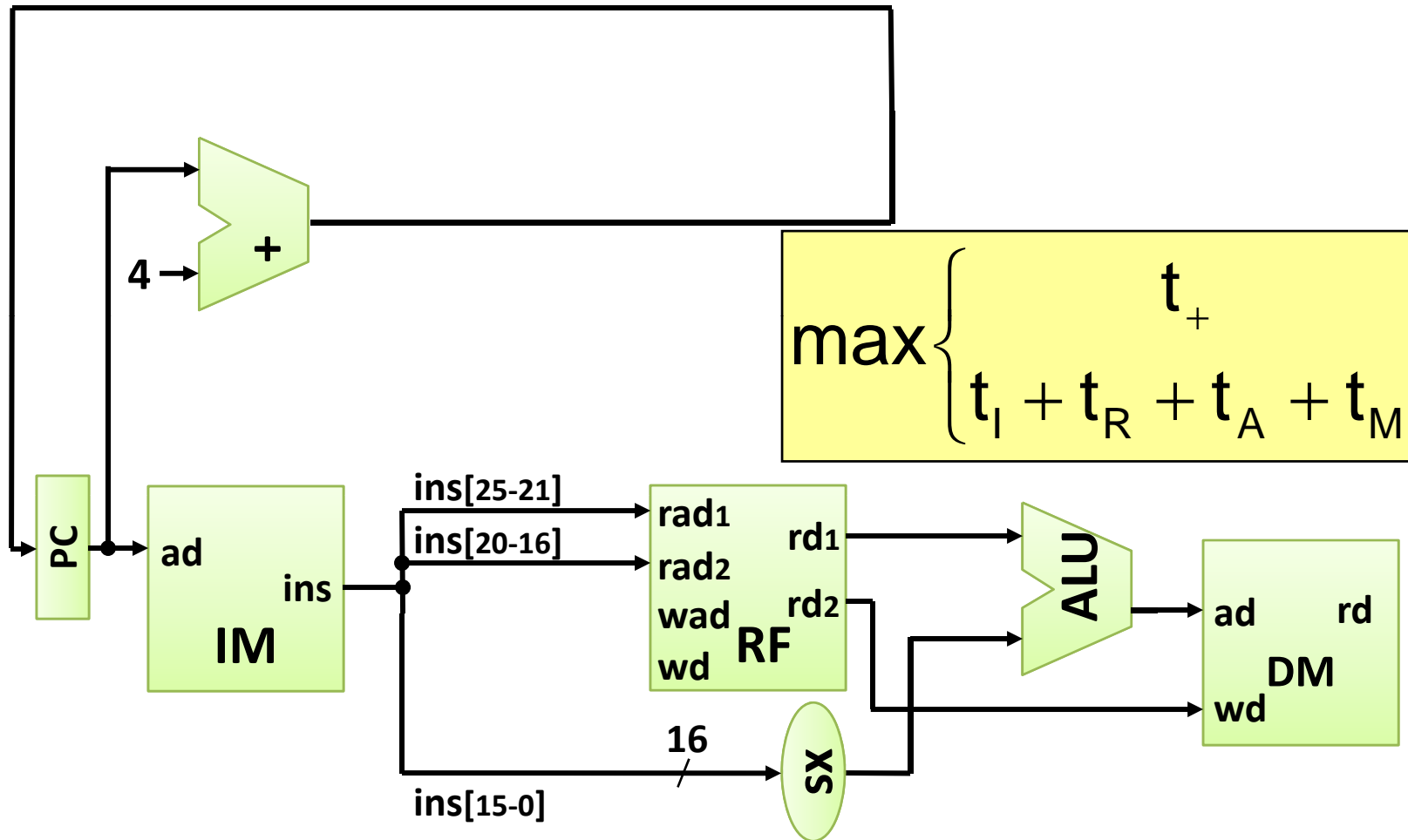


Delay for {lw}

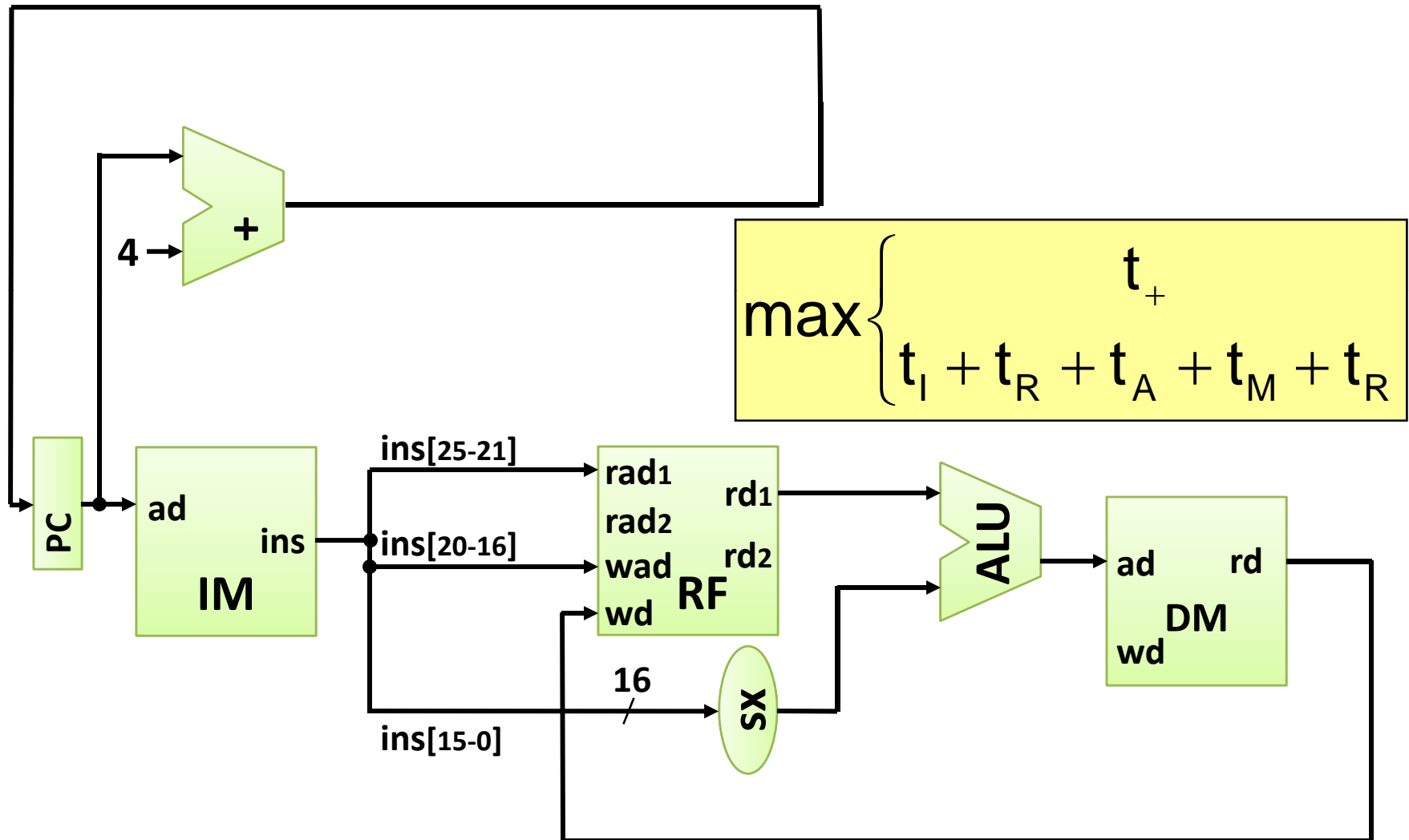

Delay for {beq}

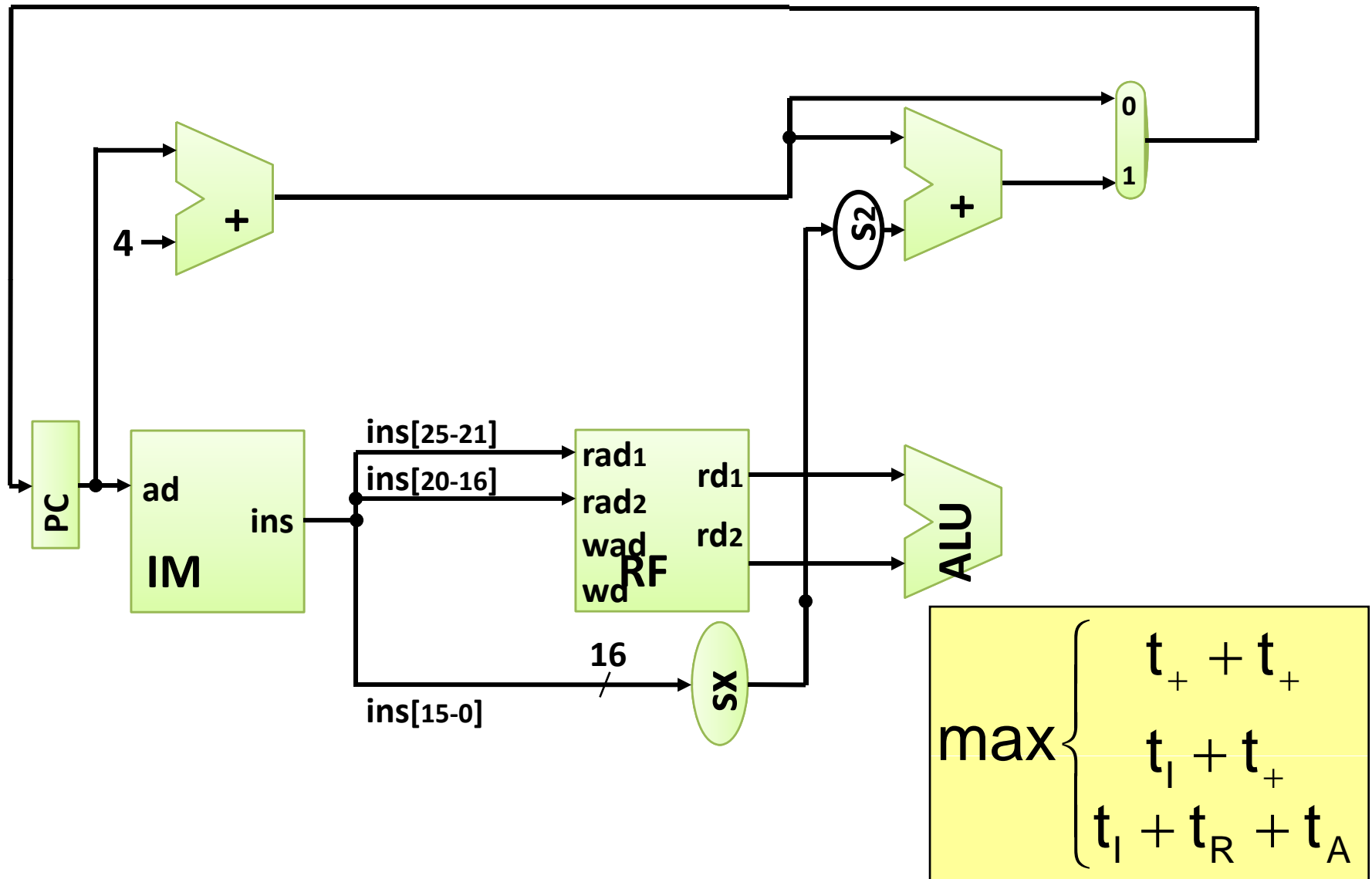

Delay for { j }

 

Overall clock period

$$\max \left\{ \begin{array}{l} R : t_+, t_I + t_R + t_A + t_R \\ SW : t_+, t_I + t_R + t_A + t_M \\ LW : t_+, t_I + t_R + t_A + t_M + t_R \\ Beq : t_+ + t_+, t_I + t_+, t_I + t_R + t_A \\ J : t_+, t_I \end{array} \right.$$

or

$$\max \left\{ \begin{array}{l} t_I + t_R + t_A + t_M + t_R \\ t_+ + t_+ \\ t_I + t_+ \end{array} \right.$$

Analyzing performance

Components	Delay	Example
Register	0	0ns
Adder	t_+	4ns
ALU	t_A	5ns
MUX	0	0ns
RF	t_R	3ns
Instruction Memory	t_I	6ns
Data Memory	t_m	6ns
Bit manipulation	0	0ns

INS	Delay
R	17ns
SW	20ns
LW	23ns
Beq	14ns
J	6ns

Thanks